
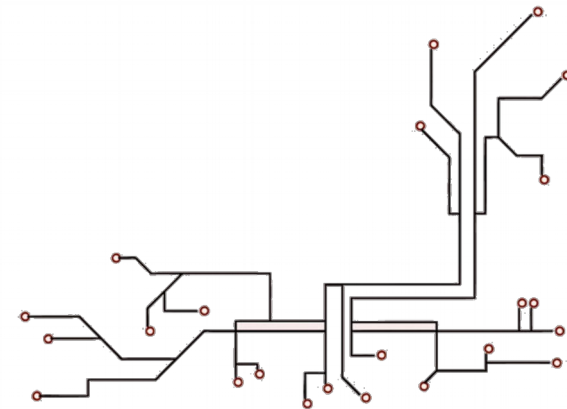


# MAKING




with

# ELECTRICITY

A POSTERIORI  
Play · Experience · Learn

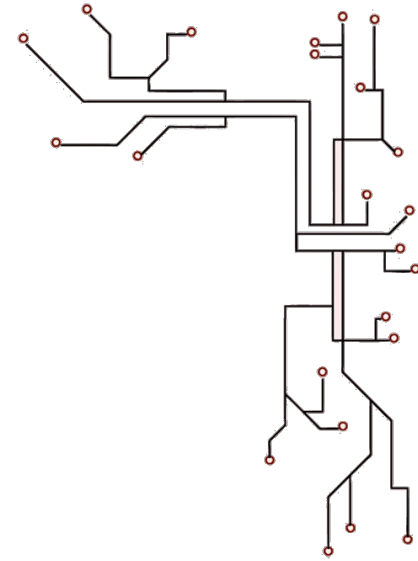



# Wire Loop Game

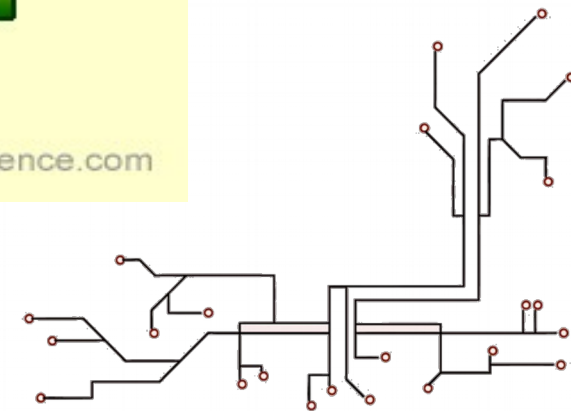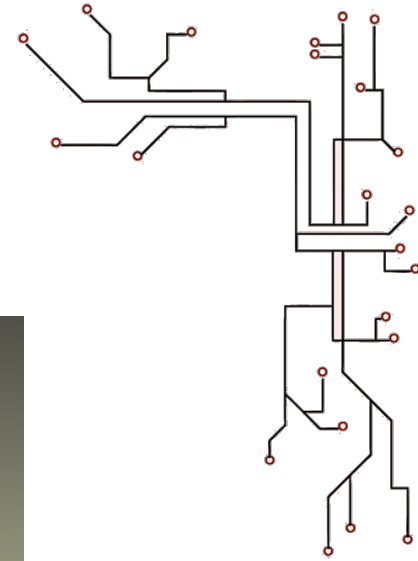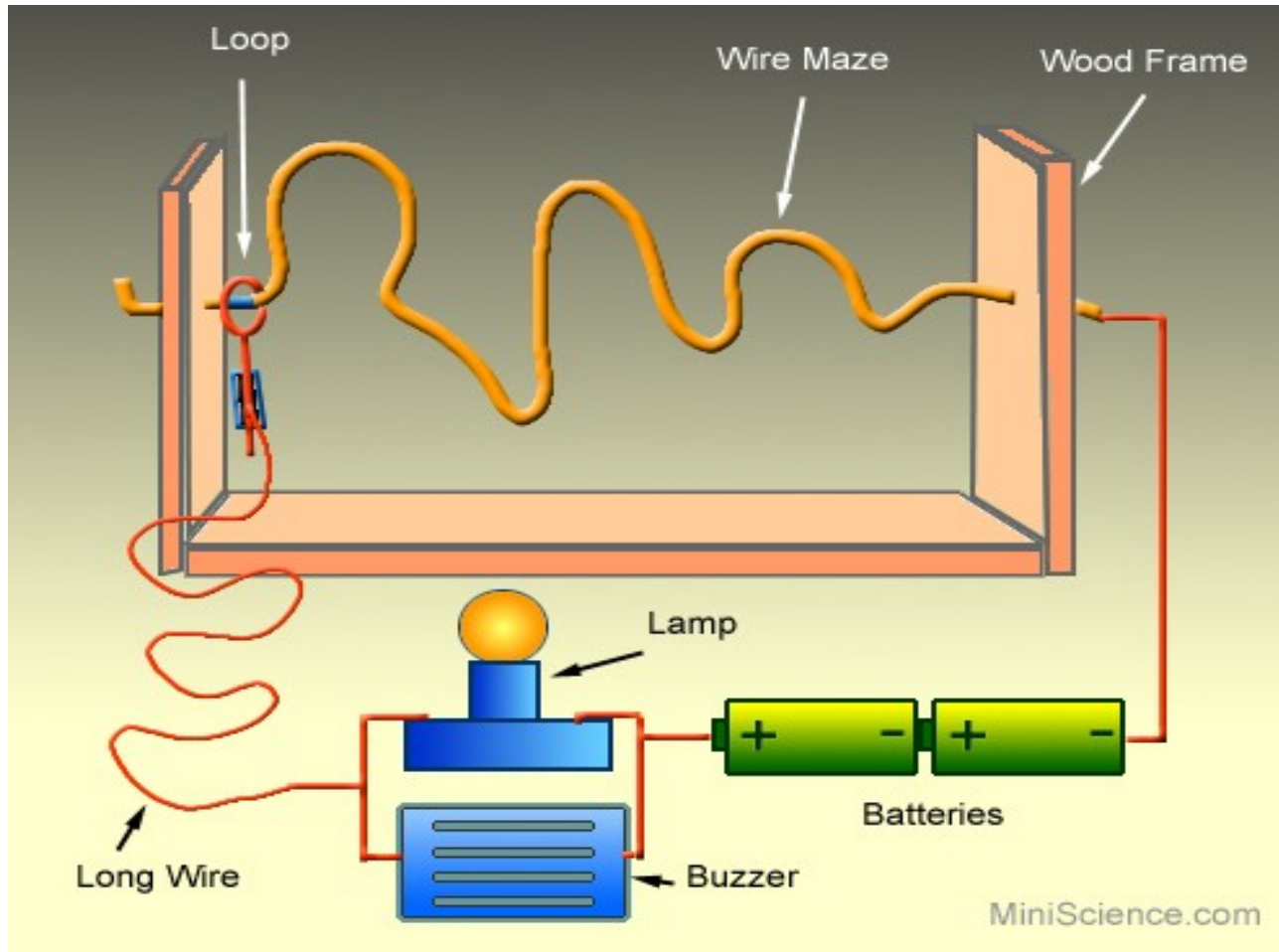



**A POSTERIORI**

Play · Experience · Learn

# Step 1 – Cut & Sand Wood


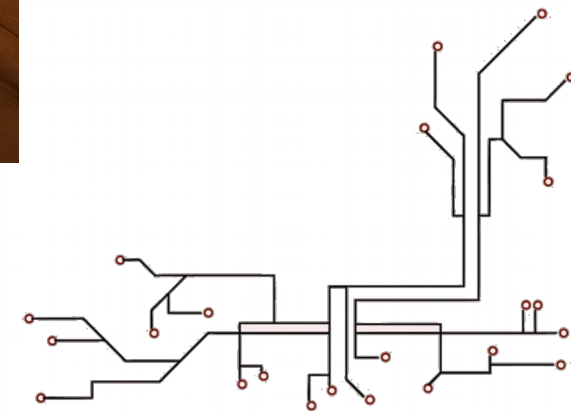
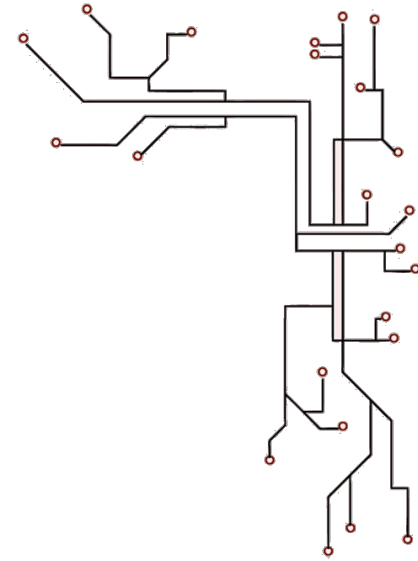


# Step 2 – Drill 2 Holes

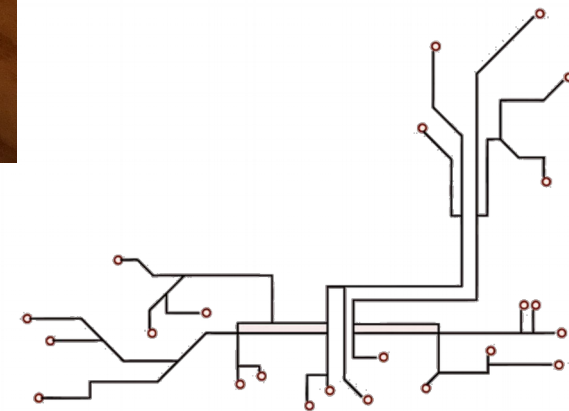
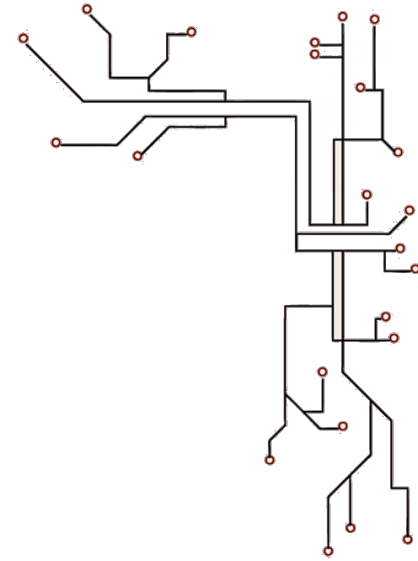



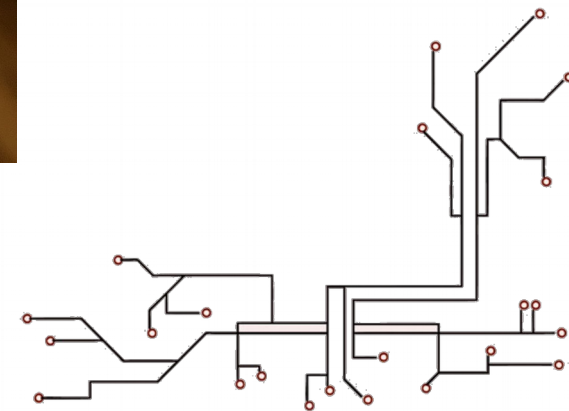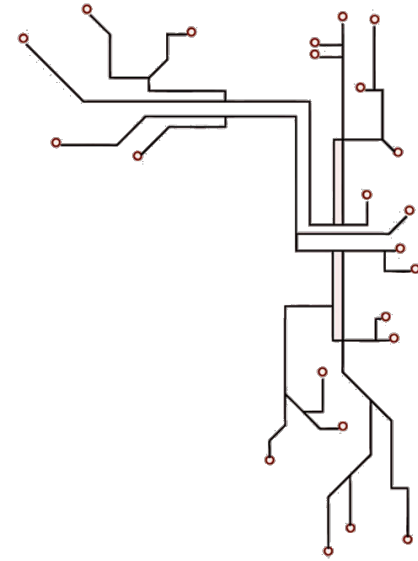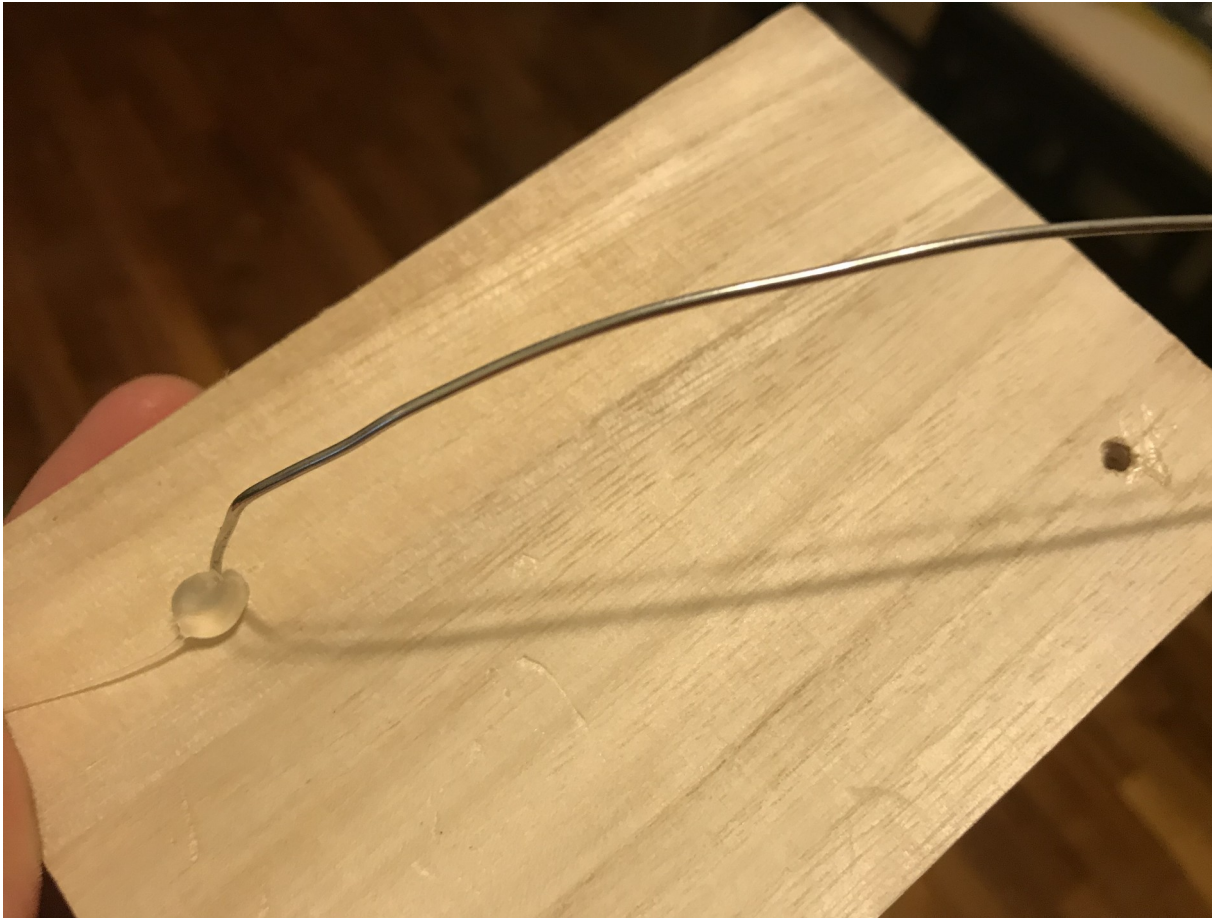
# Step 3 – Fit #18 (thick) Wire Into Hole & Hot Glue




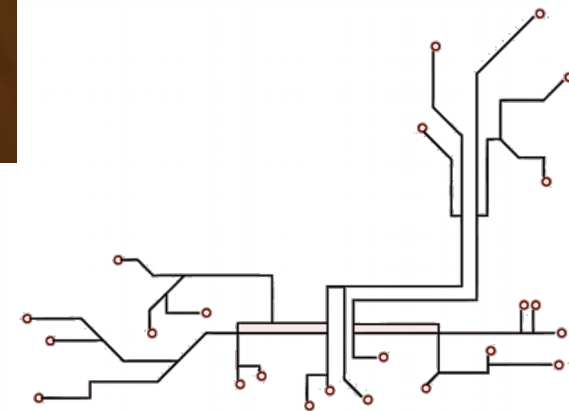
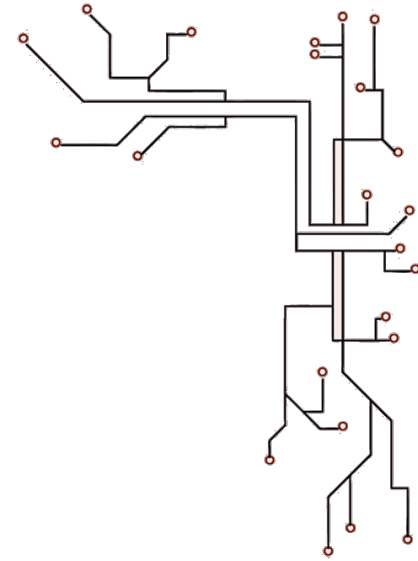
# Step 4 – Twist #16 (thin) Wire Into Loop



**A POSTERIORI**

Play · Experience · Learn
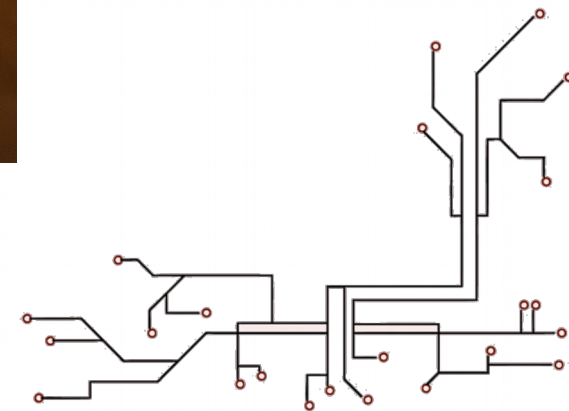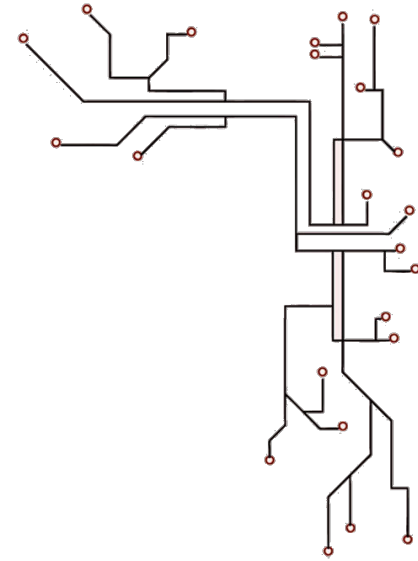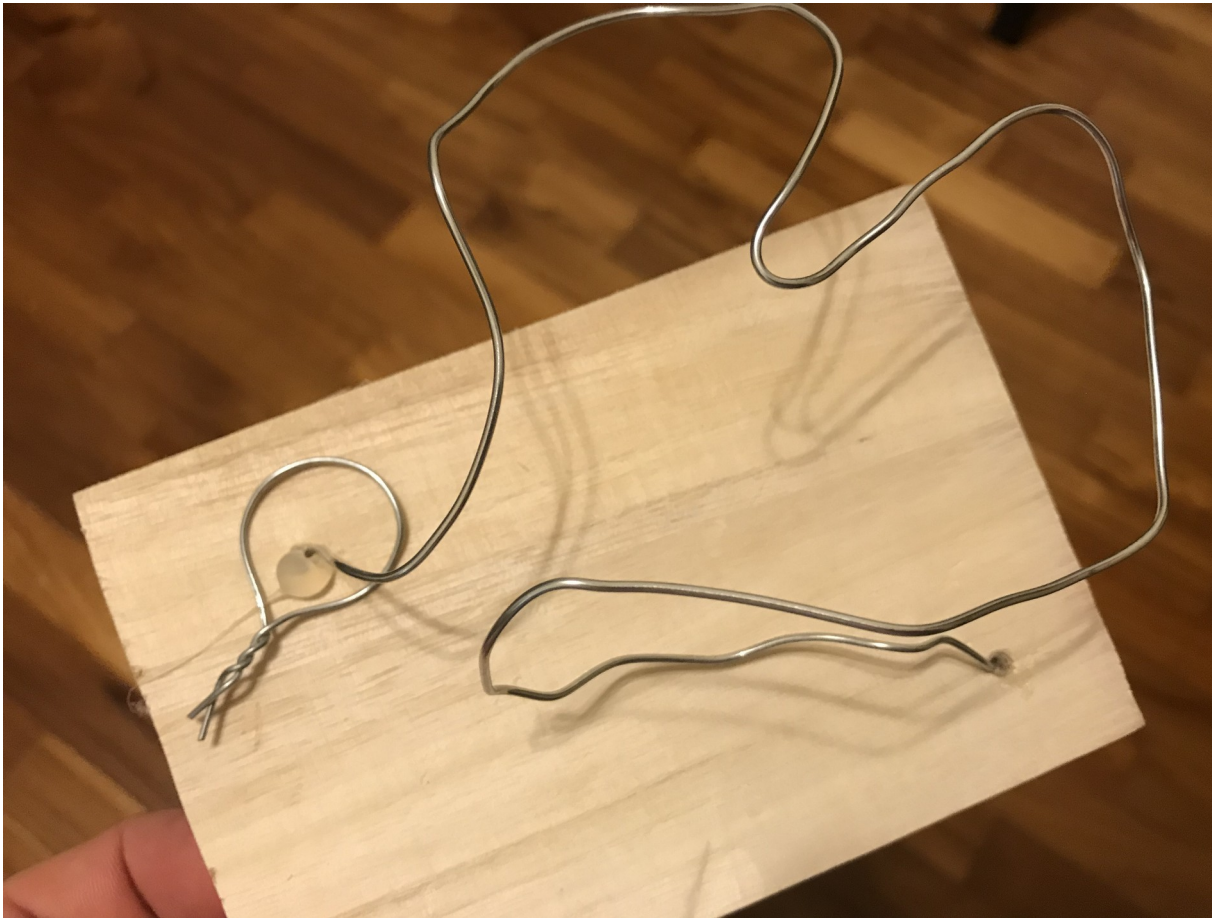
# Step 5 – Wind Loop In Wire and Hot Glue Loose End




**A POSTERIORI**




Play · Experience · Learn



# Step 6 – Stick Buzzer On Board


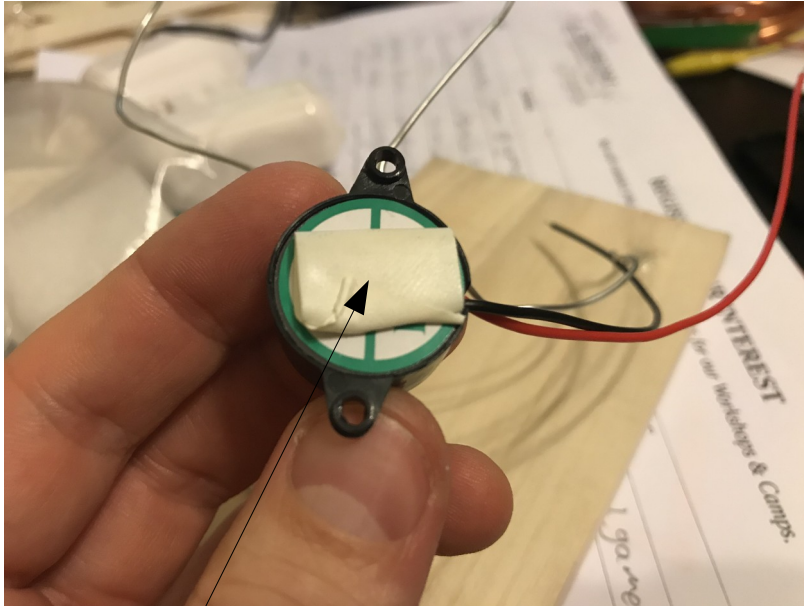


Double  
Sided Tape

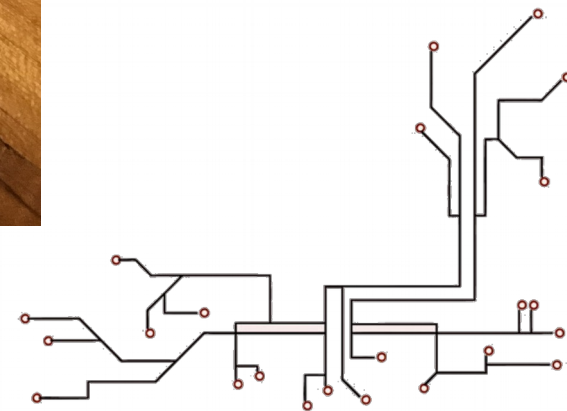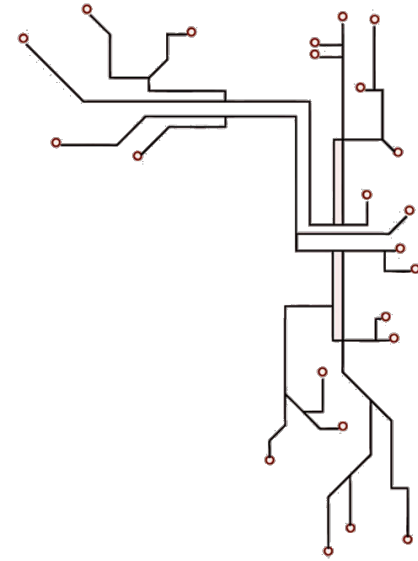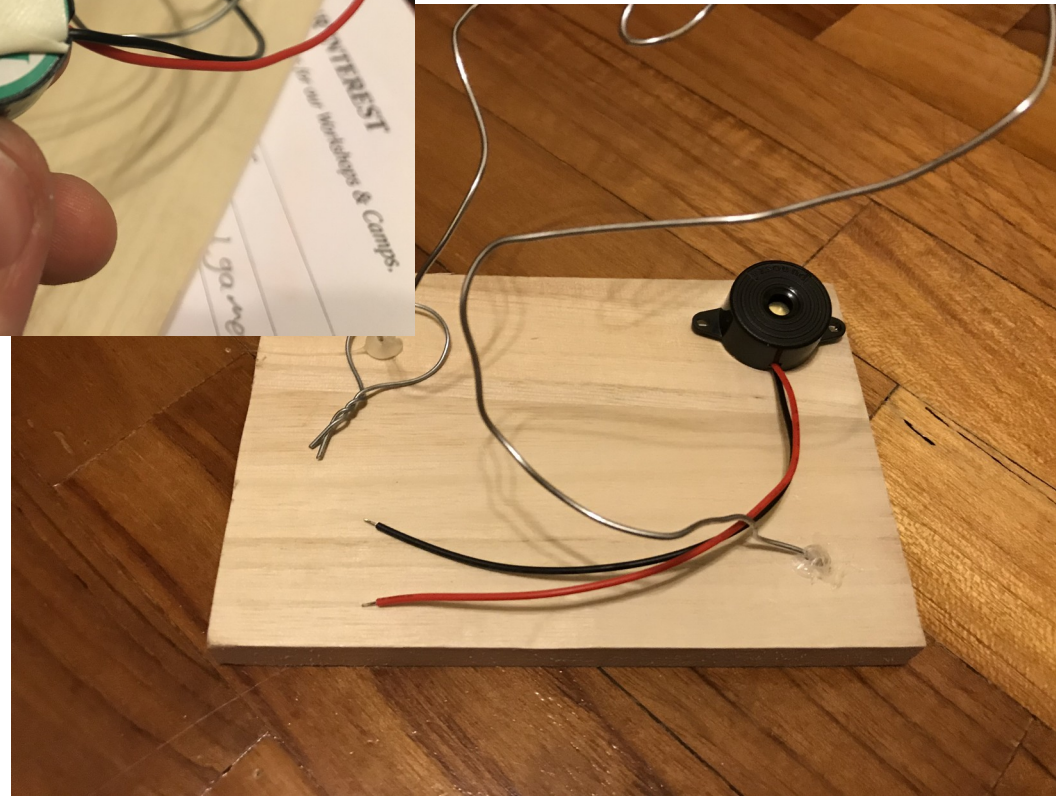




# Step 7 – Arrange Battery & Wires

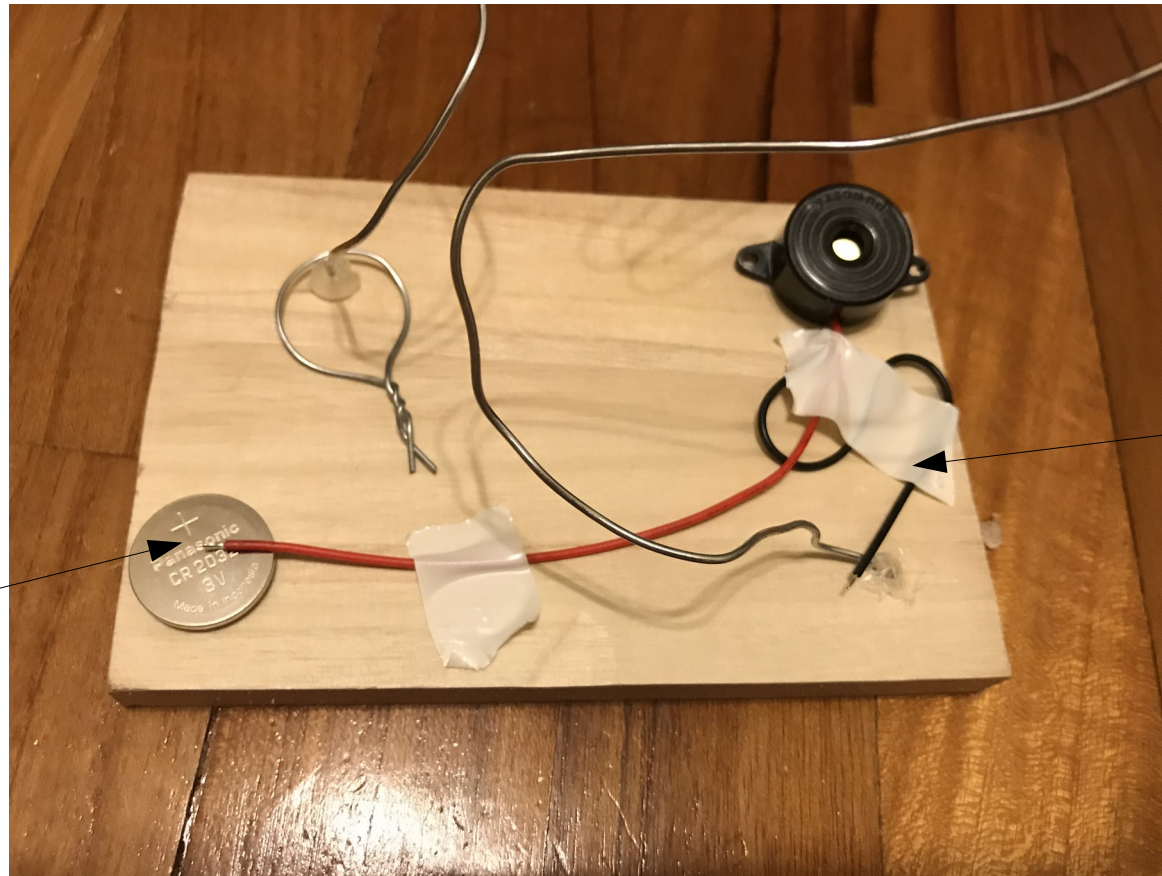
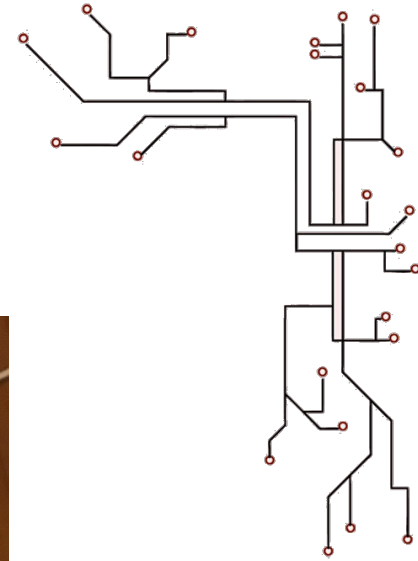


Red Wire  
To Battery +

Black Wire  
to Main  
Wire End

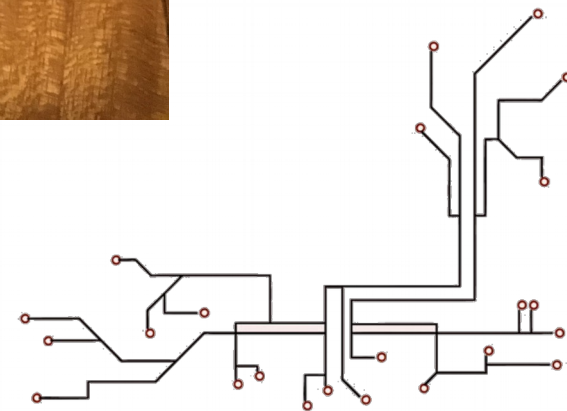

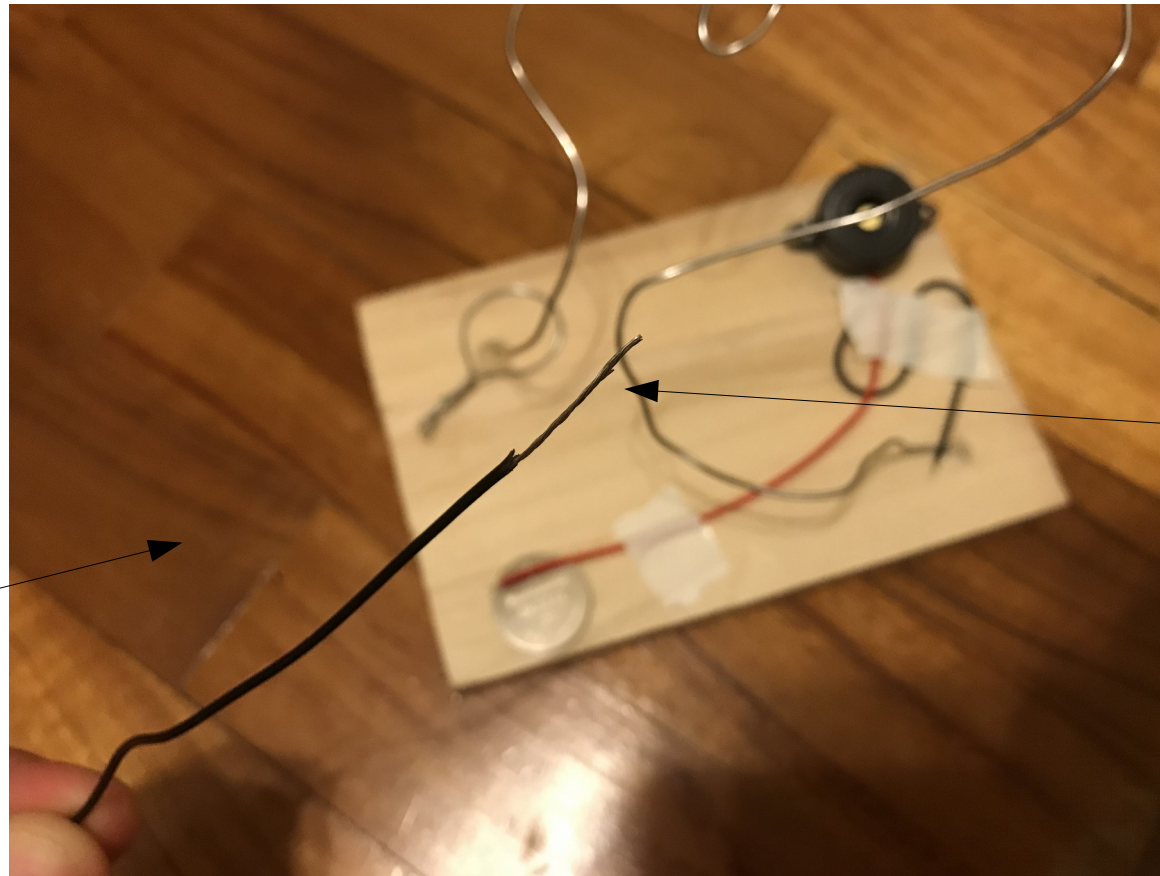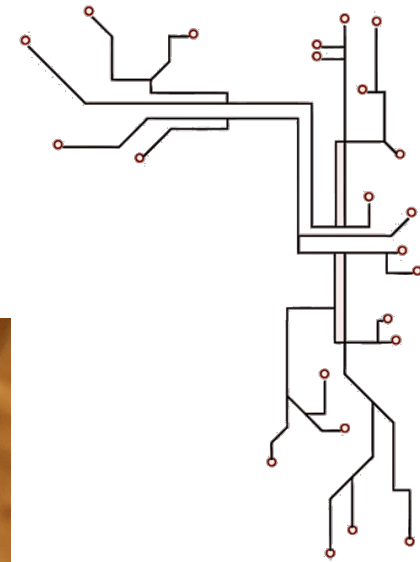
# Step 8 – Measure, Cut & Strip Handle/Wire from Loop to Battery






Black Wire  
To Battery -

Strip a  
Long  
Ending

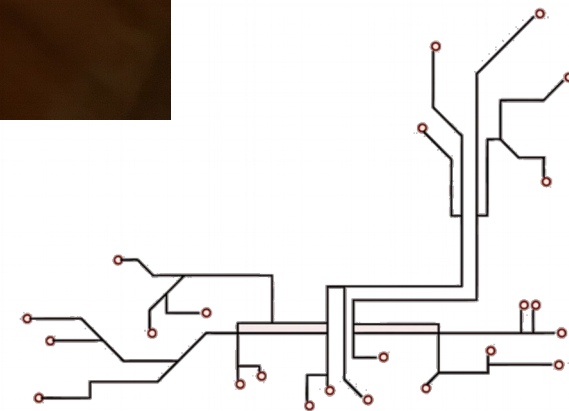

# Step 9 – Twist Black Wire End Around Loop Twist

Twist Around  
Twist


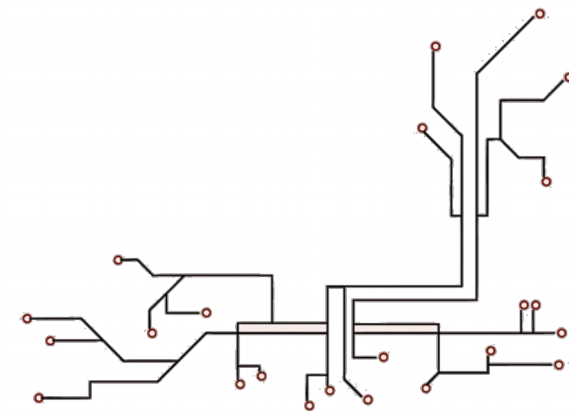
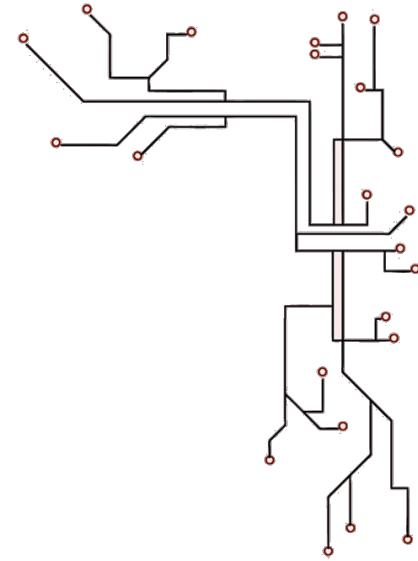
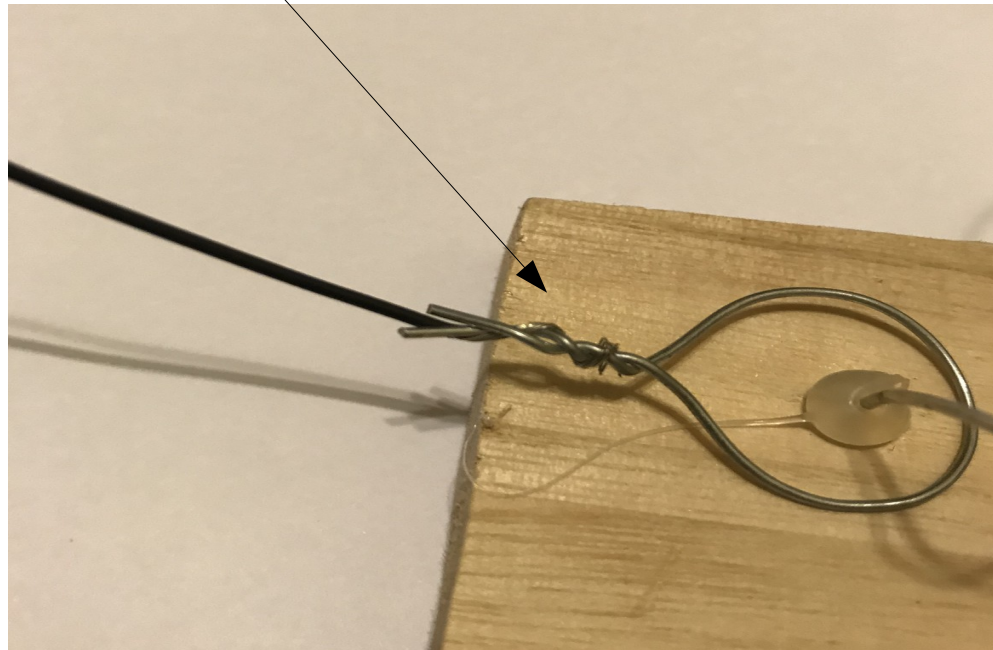


**A POSTERIORI**




Play · Experience · Learn


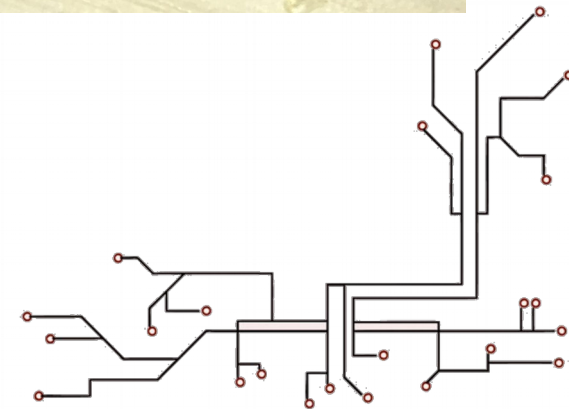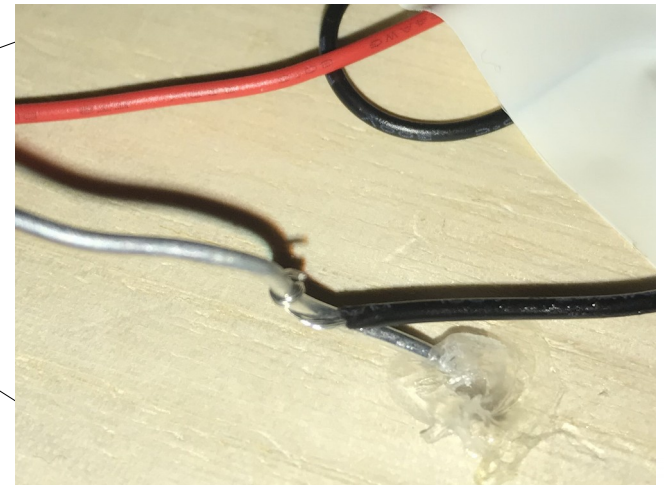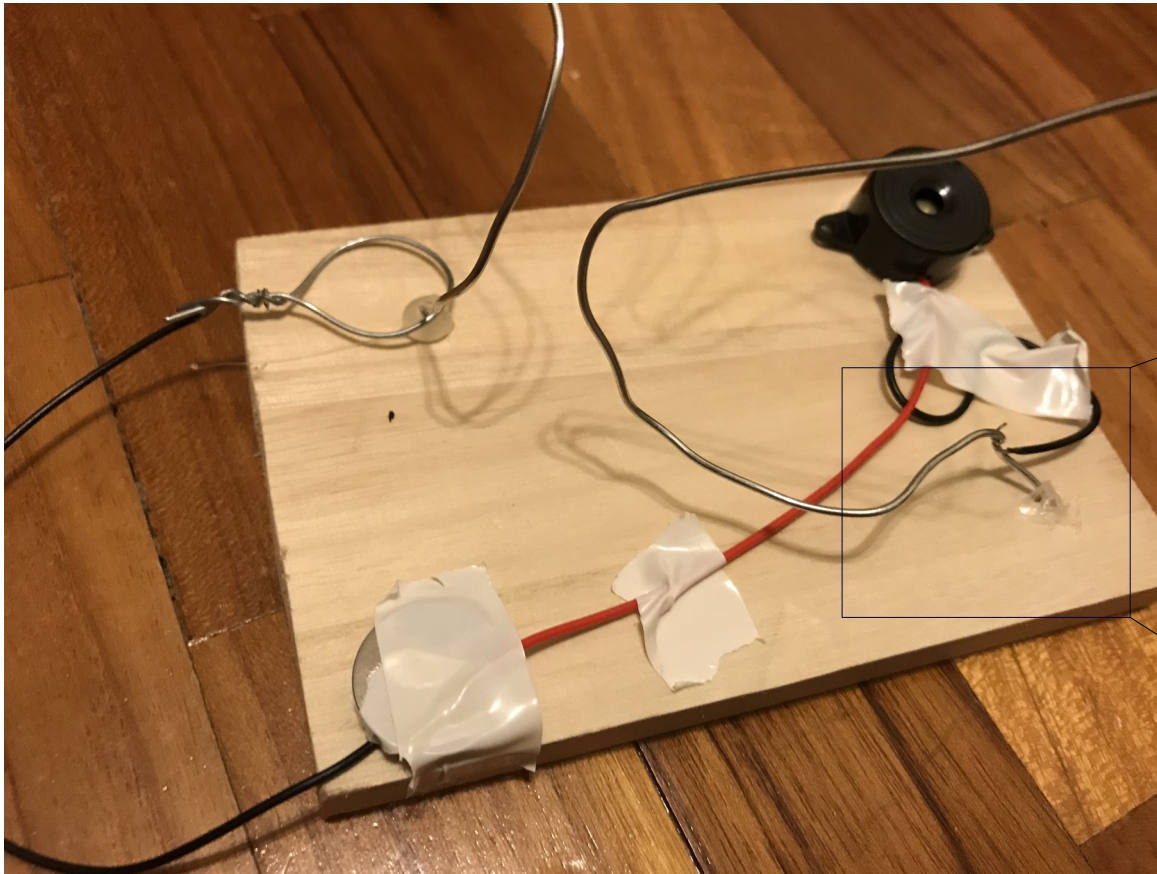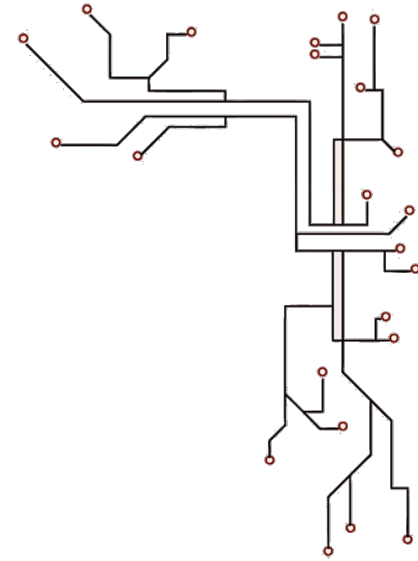
# Step 10 – Twist Buzzer Black Wire End Around Main Wire





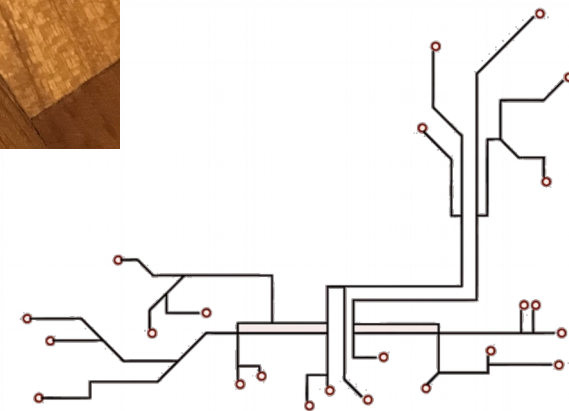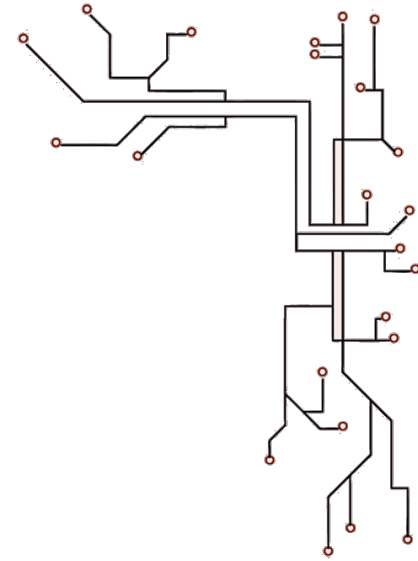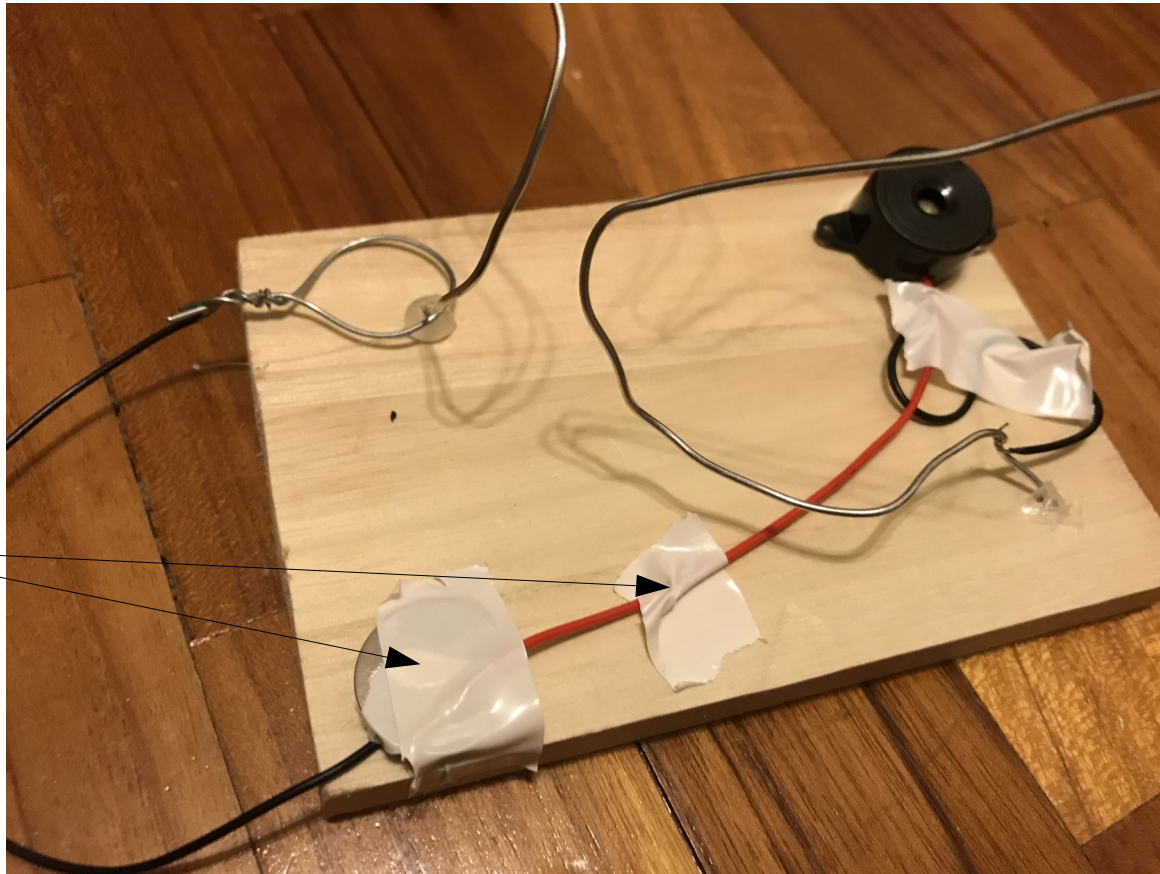
# Step 11 – Tape Buzzer Red Wire To Battery +








# Step 12 – Tape Black Wire to Battery -

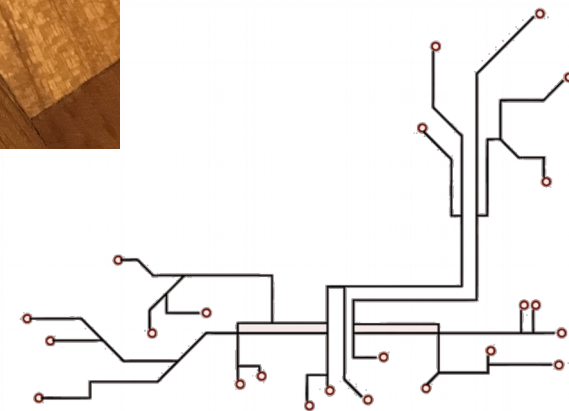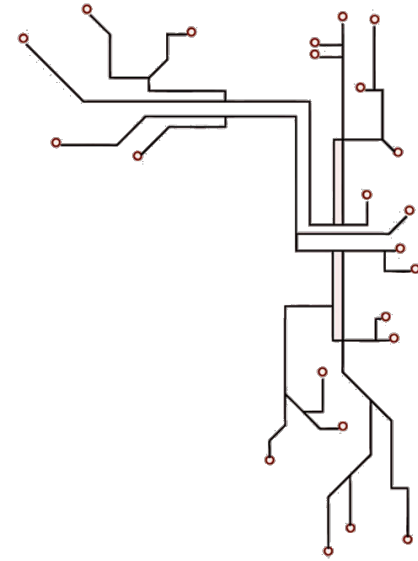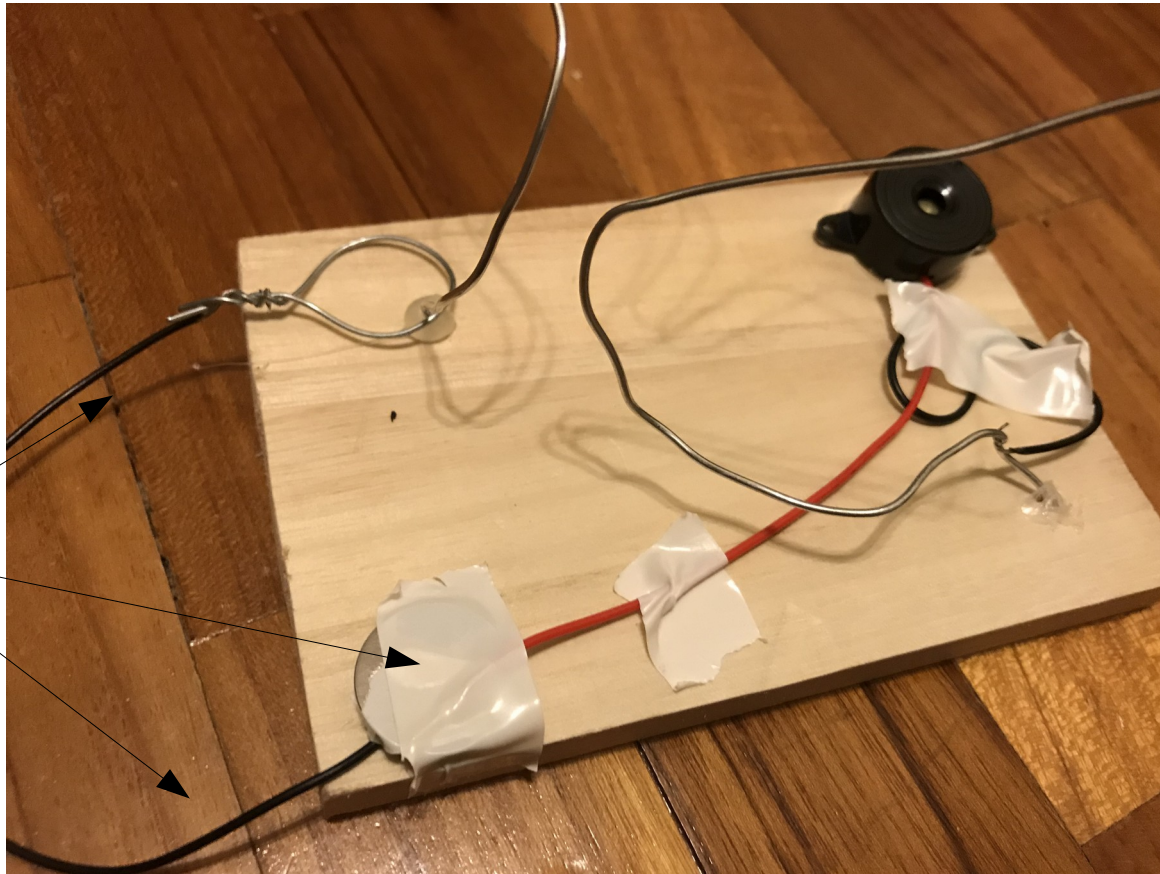



# Step 13 – Test & Play!

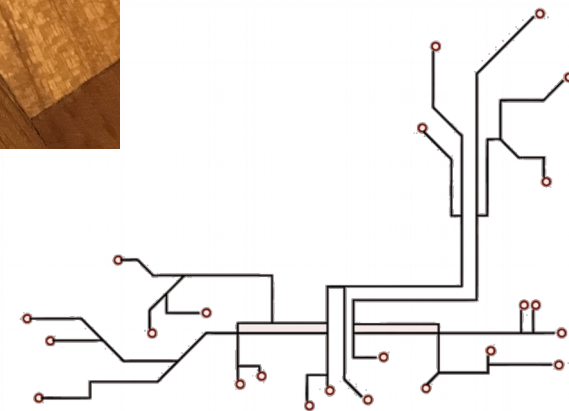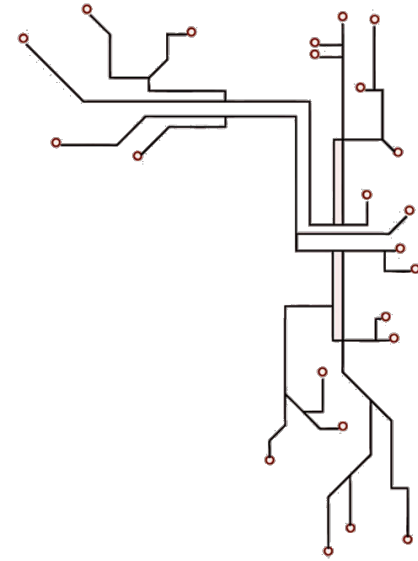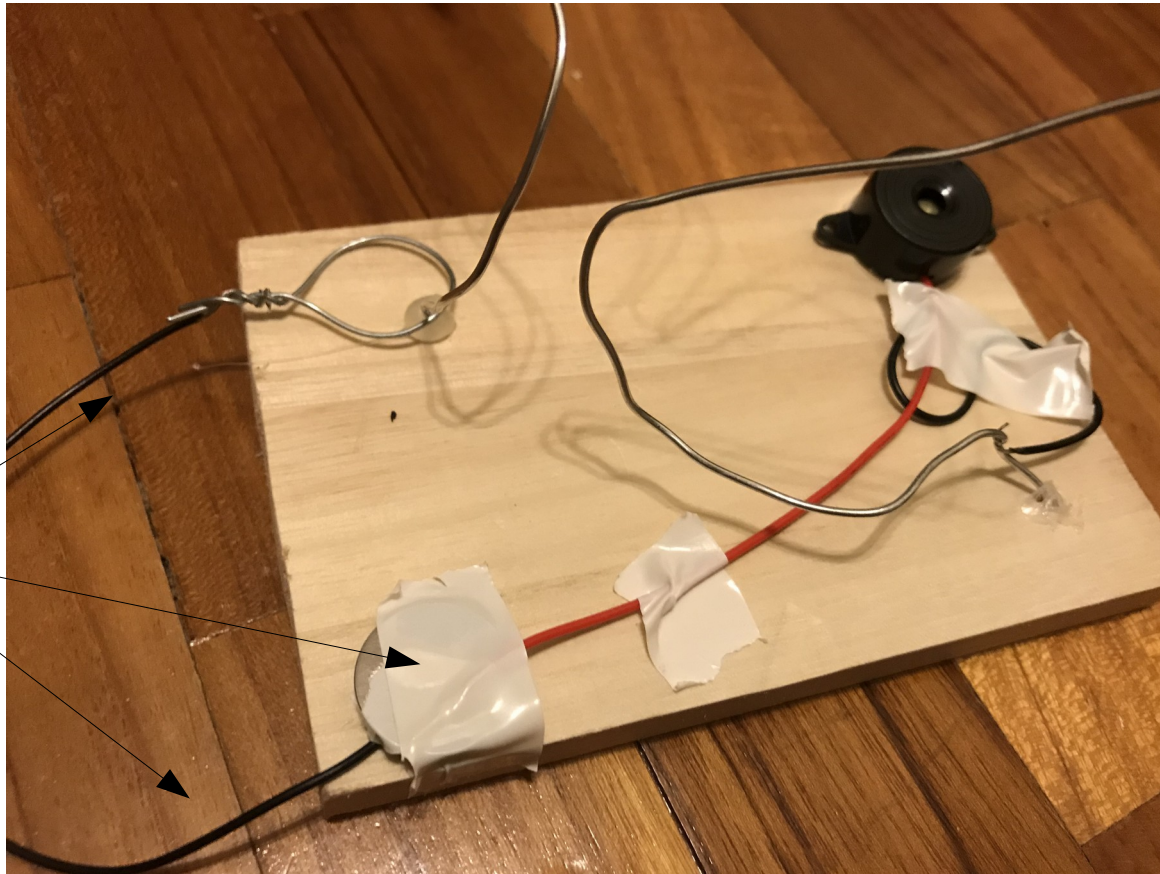

**A POSTERIORI**  
Play · Experience · Learn