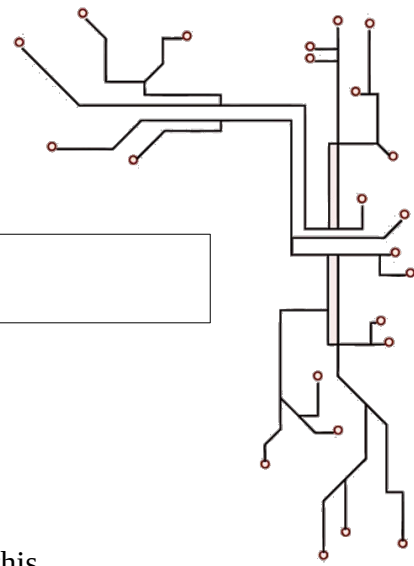


# A POSTERIORI

Play · Experience · Learn



<b>Name:</b>		<b>Class:</b>	
--------------	--	---------------	--

## Scratch + Arduino

### Before you start...

Make sure you have the **mLink** software installed. The icon should look like this...



You will also need the following hardware...


Item	Qty
Laptop	x1
USB Cable	x1
Arduino	x1
Jumper wires	A bunch
LED	x1 set
Resistors	x1 set
Push button switch	x1
Breadboard	x1

As the lessons progress, you will be provided with more hardware, but this is enough to start.
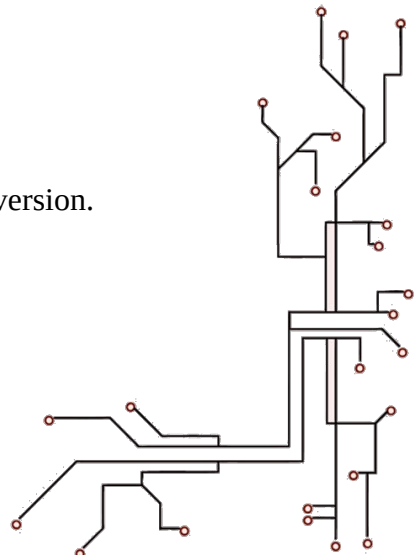
### Getting the slides...

Slides for this programme are available at <https://a9i.sg/huayi>

Your school laptops do not have LibreOffice installed, so please use the PDF version.




# A POSTERIORI

Play · Experience · Learn

## Lesson 1 (Outputs / Inputs)

### Exercise 1a (External LEDs)

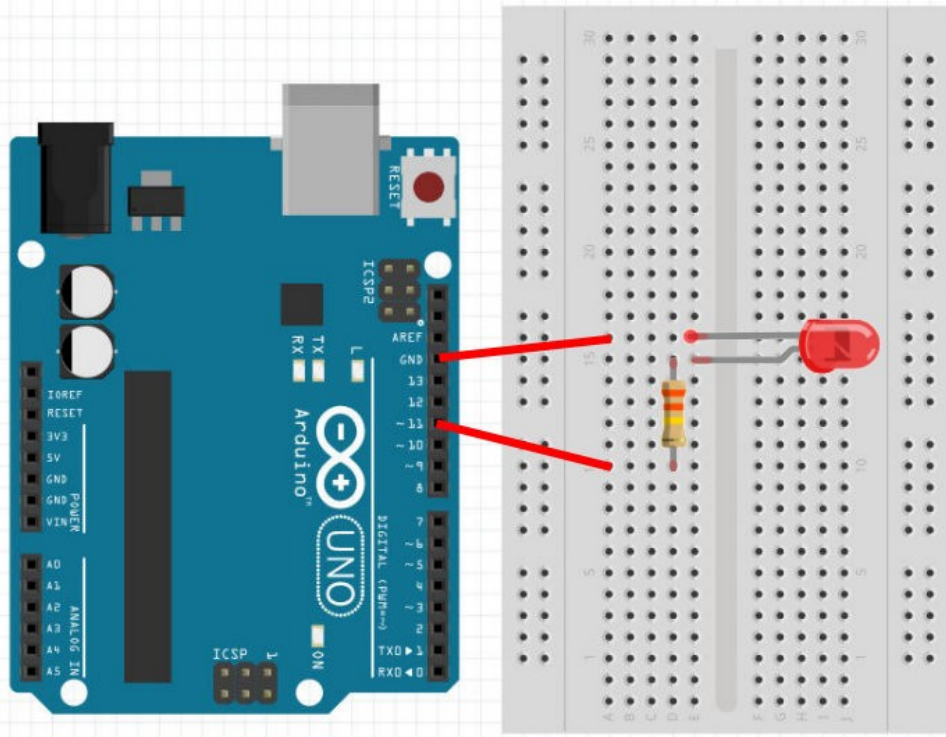

#### **LED**

Connect short leg to ground (GND) and long leg to resistor.

#### **Resistor**

Use a 330 ohms resistor. Connect one end to resistor and the other to Pin 11.

### Why have a resistor?

- Arduino pins provides 5V
- LEDs requires different voltages depending on color
  - Red, Yellow, Infra-red: 1.8V
  - Blue, White, UV: 3.3V
  - Green: Depends. Try 1.8V first.
- Resistor helps to reduce the voltage



### Challenges!

1) Modify your earlier program to control the external LED instead of the internal LED. What changes did you make?

Ans: \_\_\_\_\_

2) Program the connected LED blink continuously.

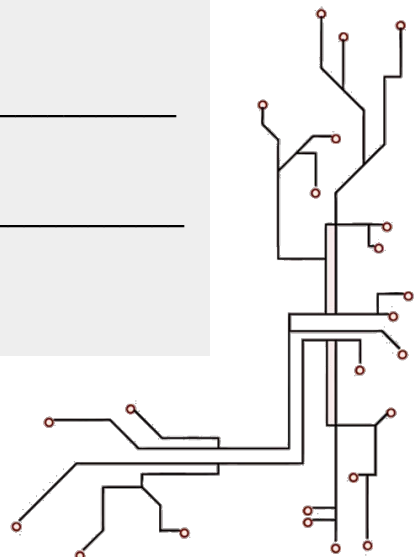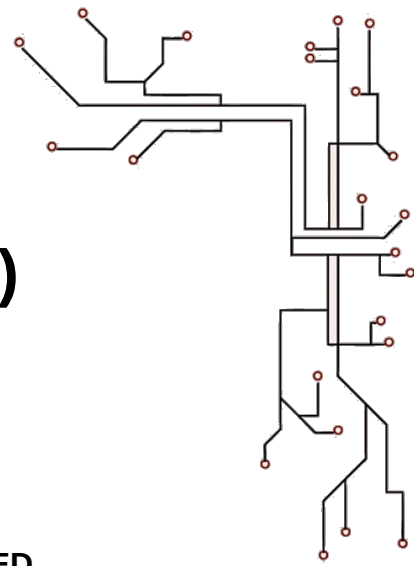
**Do this on your computer and inform the instructor when done.**



# A POSTERIORI

Play · Experience · Learn

## Exercise 1b (External Inputs)



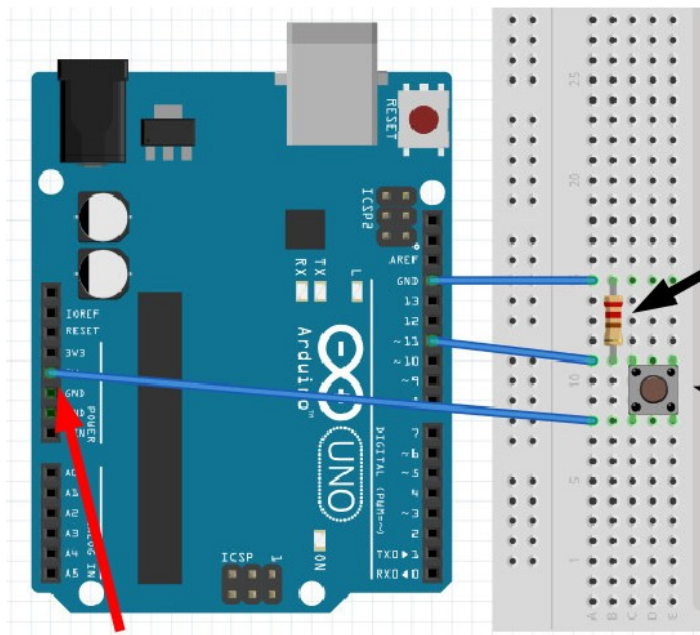


Connected to 5V

Make these connections

**Resistor**  
Value isn't as important as before. Recommend to pick 1000 ohm, but most other values will do as well.

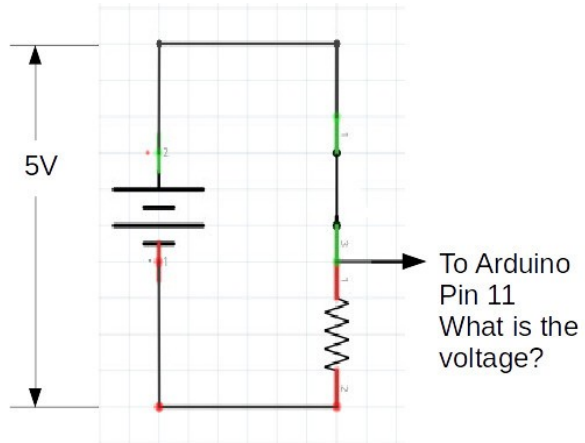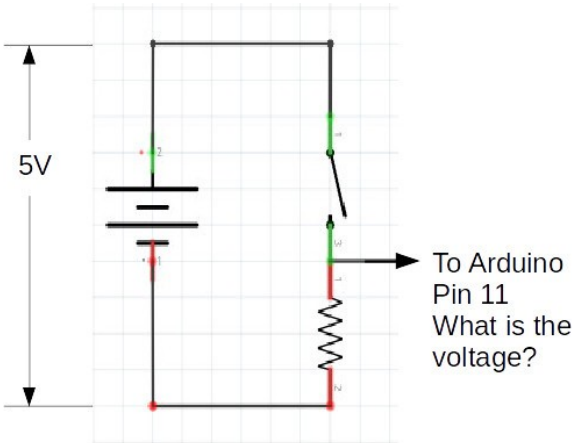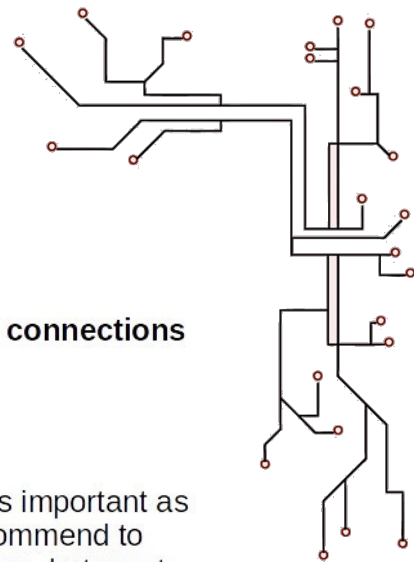**Push button switch**  
Connects the top and bottom when pressed




### Switch Open

- Pin 11 is connected to 0V via the resistor
- Pin 11 not connected to 5V
- Voltage of pin 11:
  - = 0 V
  - = False
  - = Low

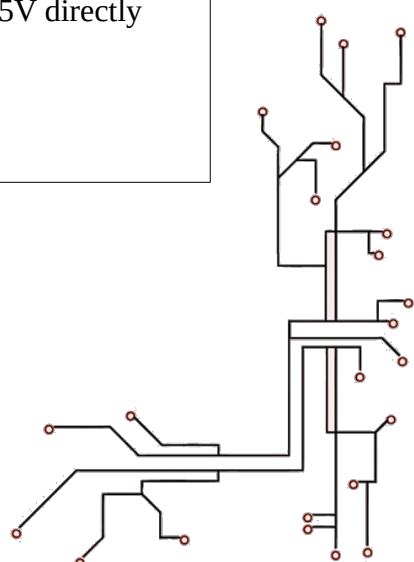
### Switch Closed

- Pin 11 is connected to 0V via the resistor
- Pin 11 is connected to 5V directly
- Voltage of pin 11:
  - = 5 V
  - = True
  - = High



# A POSTERIORI

Play · Experience · Learn

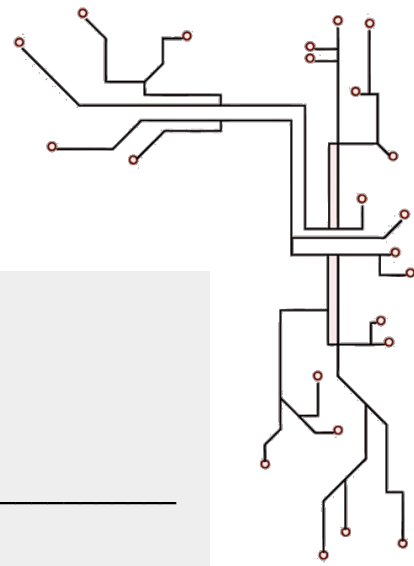

## Why?

Why can't we connect the switch directly to ground without a resistor?

Ans: \_\_\_\_\_

\_\_\_\_\_

Add this script to your "Device"



Add this script to your "Sprite"



## Challenges!

- 1) Make an LED blink rapidly for 2 seconds when the button is pressed
- 2) Make an LED toggle between on and off when the button is pressed

**Do these on your computer and inform the instructor when done.**

