

What is an Arduino?




Short Answer:
This is an Arduino...




A POSTERIORI
Play · Experience · Learn

What is an Arduino?

- First we'll need to know what is a “micro-controller”

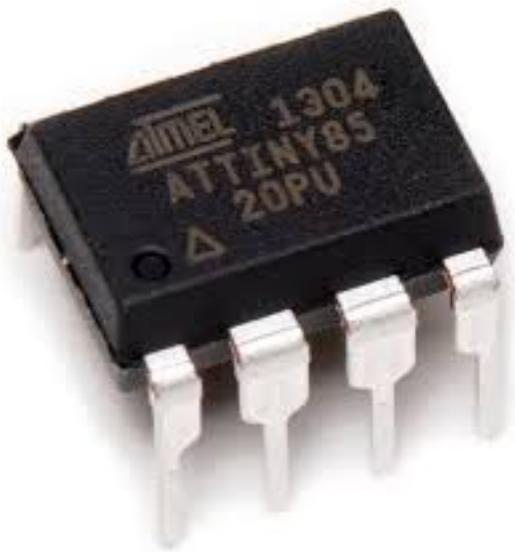

ATtiny 85

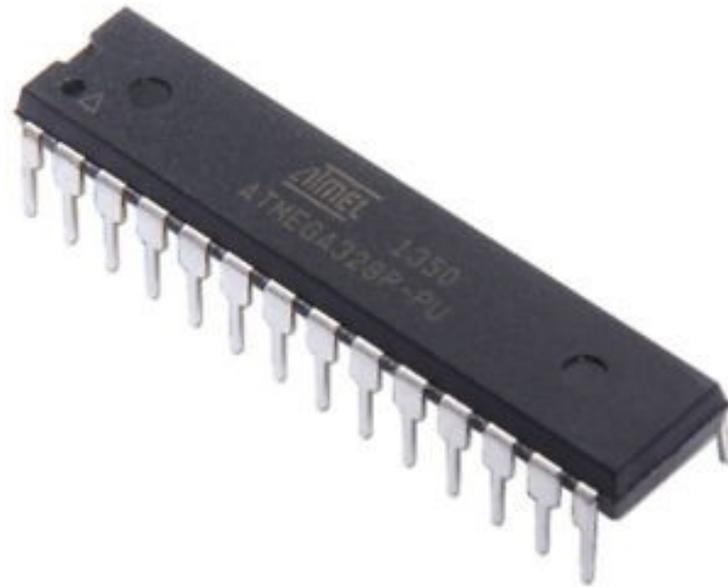


ATmega 328

What is an Arduino?

Micro-controllers are...

Like a miniature computers...

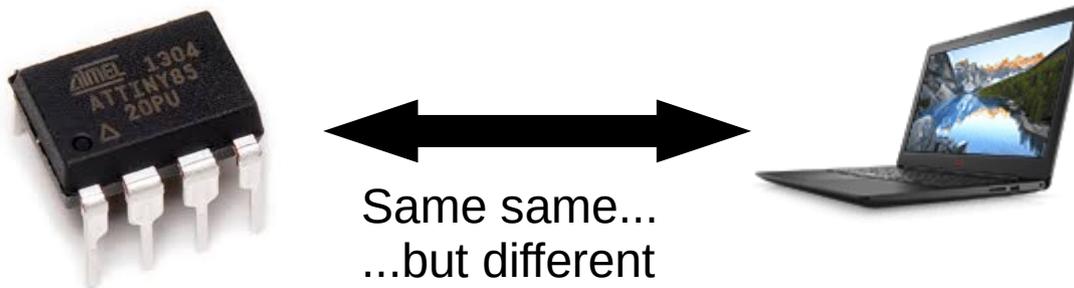- Contains processor, RAM, storage, and more
- Can be programmed like a computer




Unlike a computer...

- Provides direct electrical connection to external devices
- Can't run Minecraft or Fortnite...

What is an Arduino?

Micro-controllers can be a pain...

- Require a special device to program...

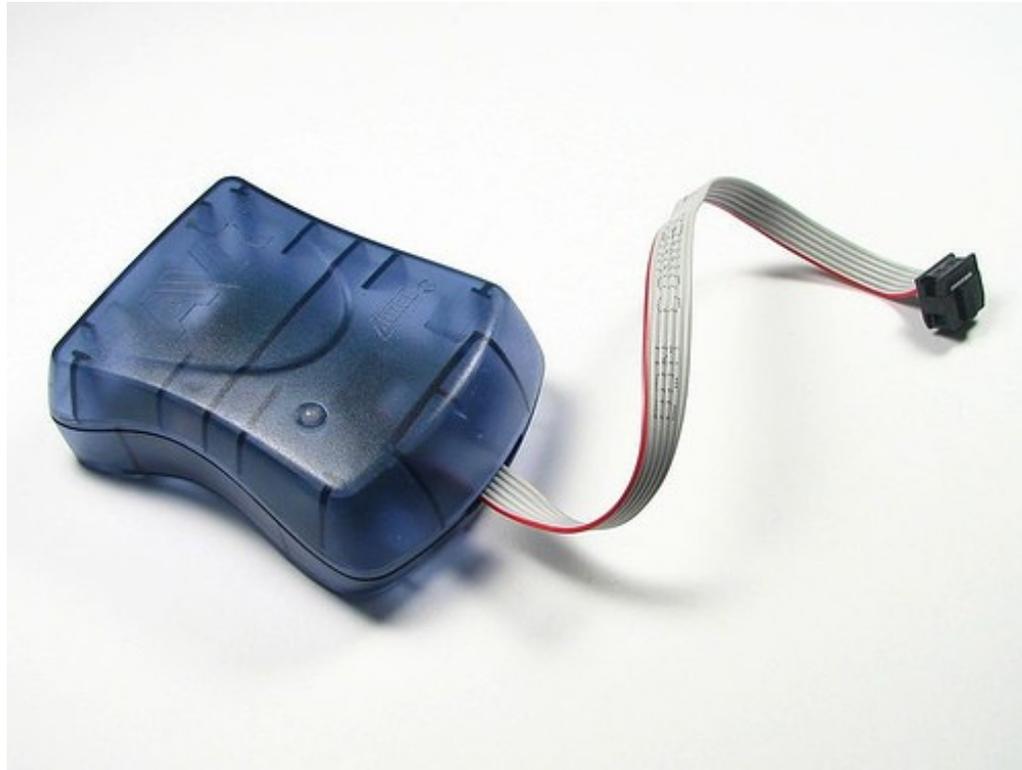

AVRISP (In-System Programmer)

What is an Arduino?

Micro-controllers can be a pain...

- Difficult to read code, that's different depending on the model...

```
// Enable ADC in single mode and slow clk pre-scaler.
ADMUX = _BV(REFS0) | _BV(MUX2) | _BV(ADLAR);
ADCSRA = _BV(ADEN) | _BV(ADPS2);

ADCSRA |= _BV(ADSC); // Trigger read

while (ADCSRA & _BV(ADSC))
    ; // Wait for completion

temperature = (float) ADCL / 256.0;
temperature += ADCH;
```

Code for ATmega8
(Doesn't work for all microcontrollers)

```
temperature = analogRead(sensorPin);
```


Code for Arduino
(Work on all Arduinos)

Both of these codes do the same thing!

What is an Arduino?

Micro-controllers can be a pain...

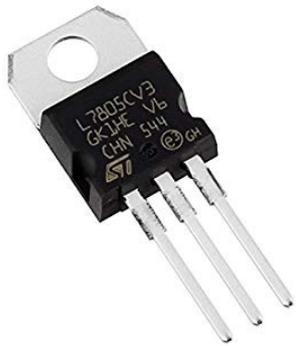- Require external parts to work (eg. voltage regulator, crystal oscillator, decoupling capacitors)



Voltage Regulator
(...this is the
simple type)



Crystal Oscillator



Capacitor

What is an Arduino?

So what is an Arduino?

- Combines a micro-controller with all the other components into a single device




Exercise 1a

External LEDs

A POSTERIORI
Play · Experience · Learn

Breadboard

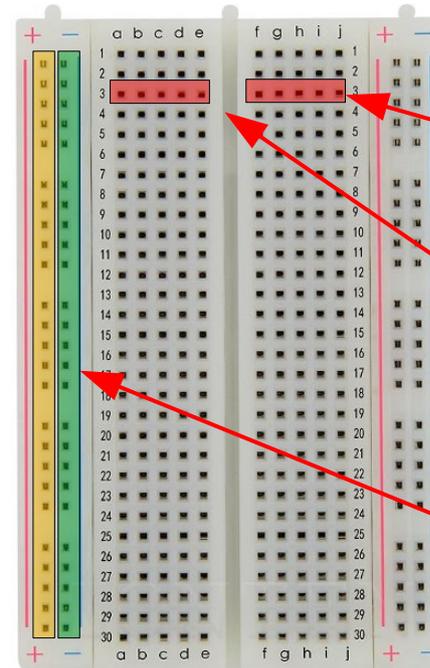
- Helps to make electrical connections
- Many components (eg. LEDs) can be plugged in directly
- Use dupont wires to make connections



Holes in the same row are connected

No connection across center gap

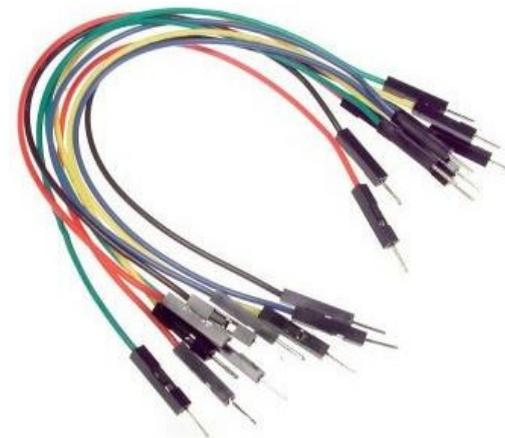
Holes by the side are connected vertically across entire board





Dupont wires
The colors doesn't matter; they all work the same

LED

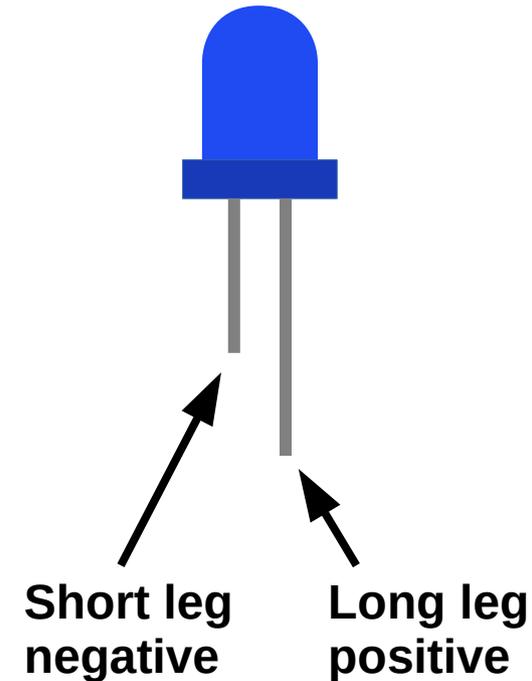- Light Emitting Diode
- Longer leg connects to positive
- Shorter leg connects to ground (0V)
- **Doesn't work if connected in reverse**



Connecting an LED

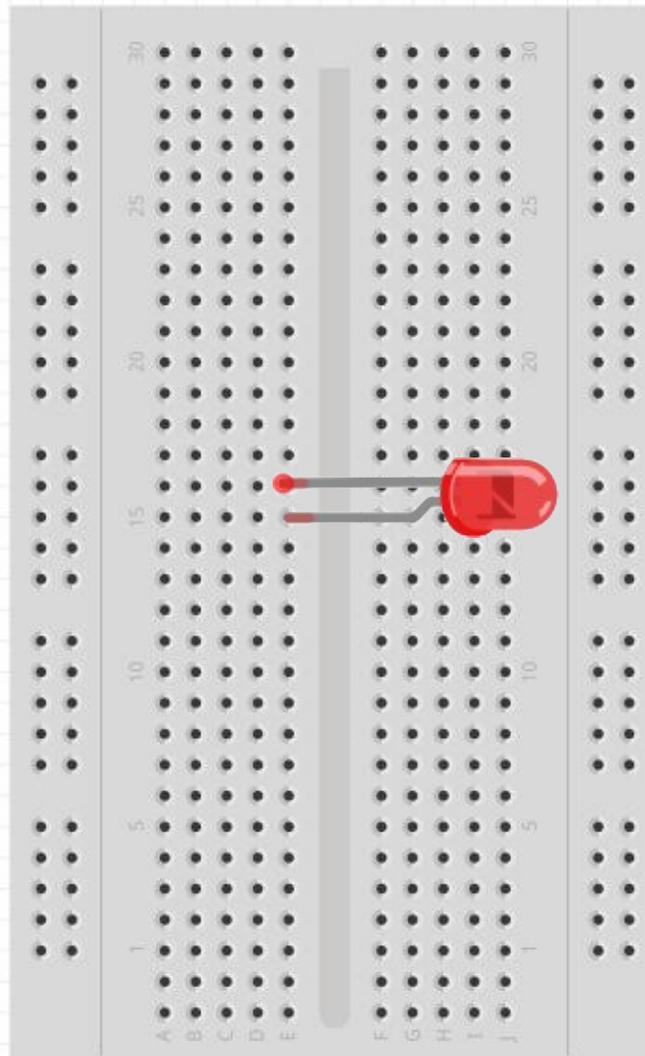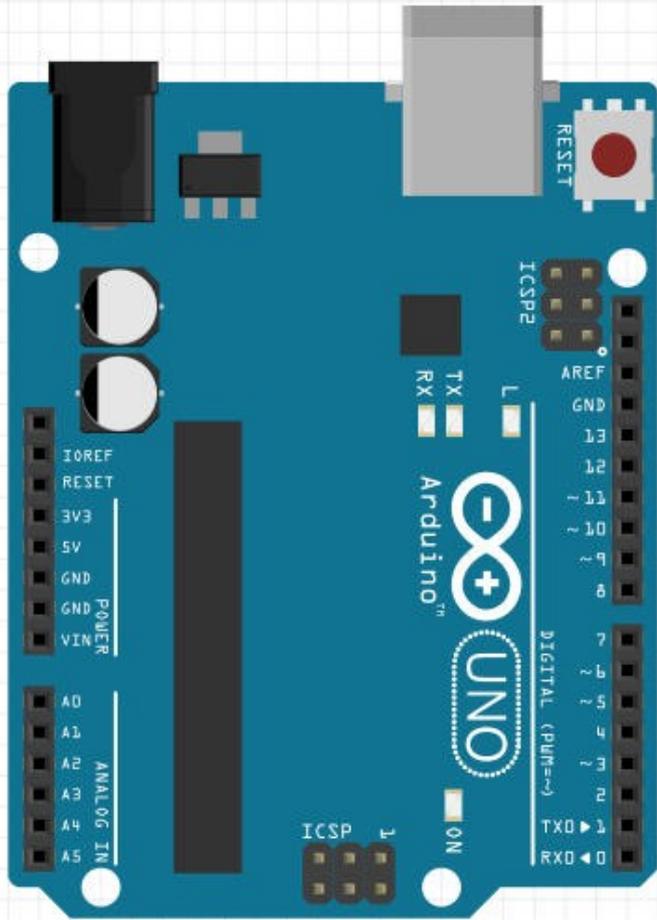


Important!!!

Take note of which leg of the LED is longer

In this example, the bottom leg is longer.

Long leg : Positive
Short leg : Gnd



Connecting an LED

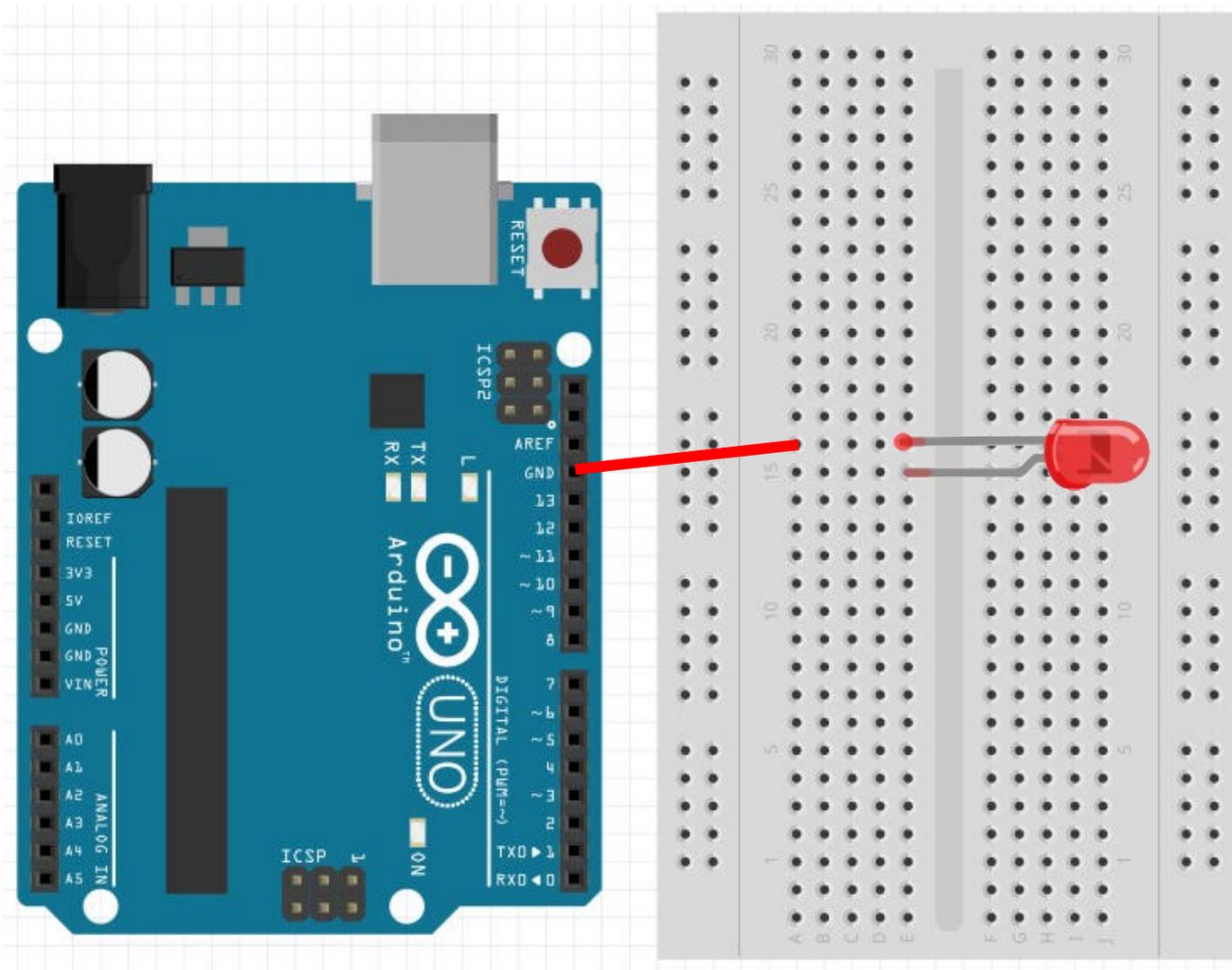

Connect a wire from "GND" to the shorter LED leg.

* My shorter leg is on top.

Connecting an LED

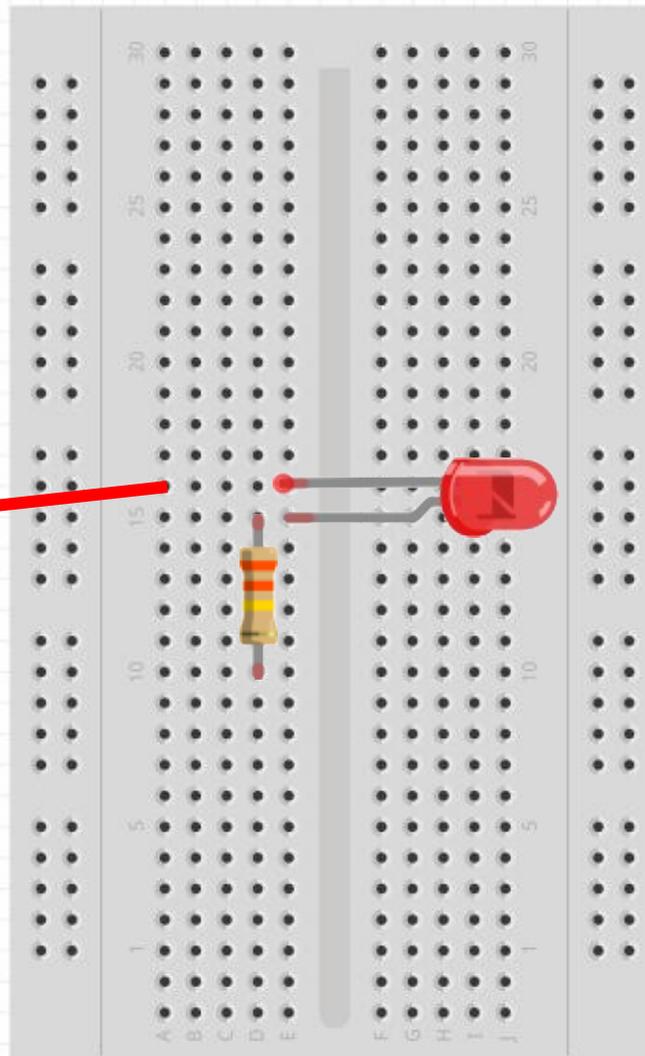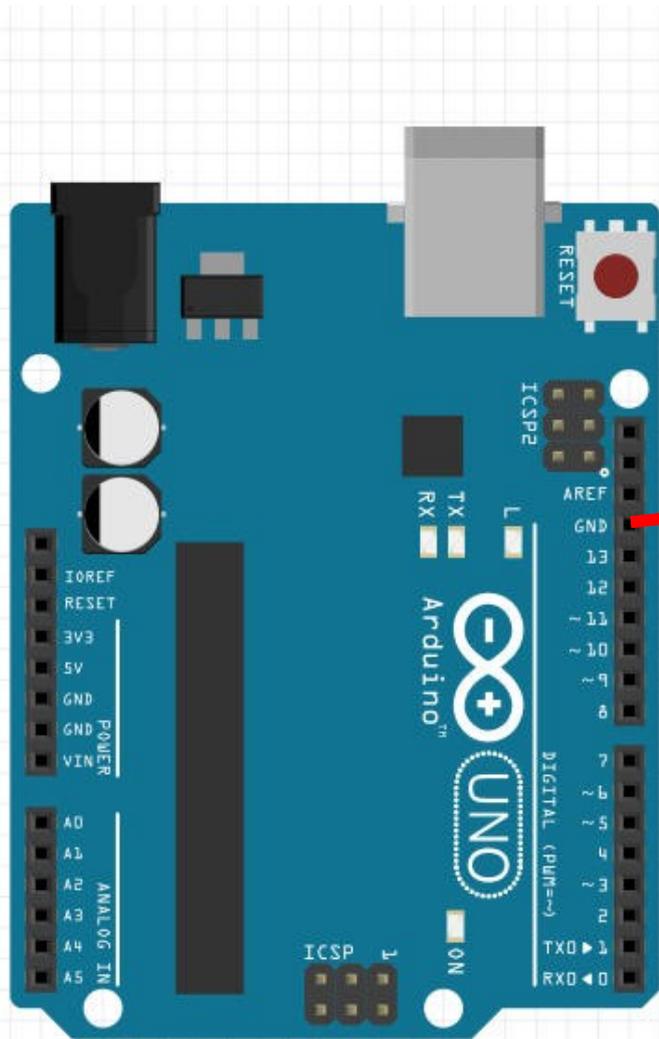

Add a resistor.

Connect one end to the long LED leg, and the other end to an empty row.




E12 Range, Resistor 330Ω, 5% Tolerance, Carbon Film

WWW.IAMTECHNICAL.COM

Orange Orange Brown Gold


Connecting an LED

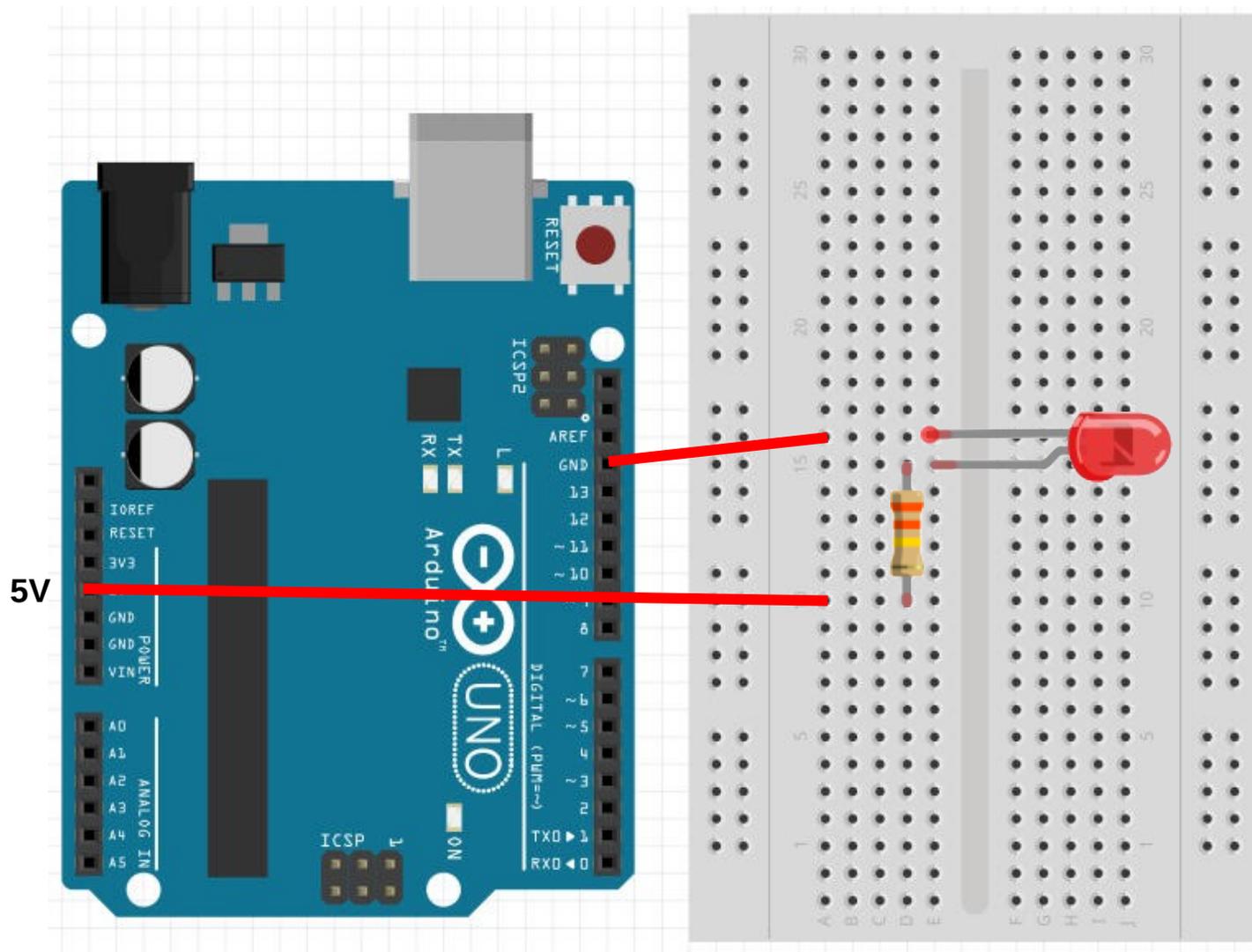

Connect the other end of the resistor to the “5V” pin

The LED should light up immediately!

Connecting an LED

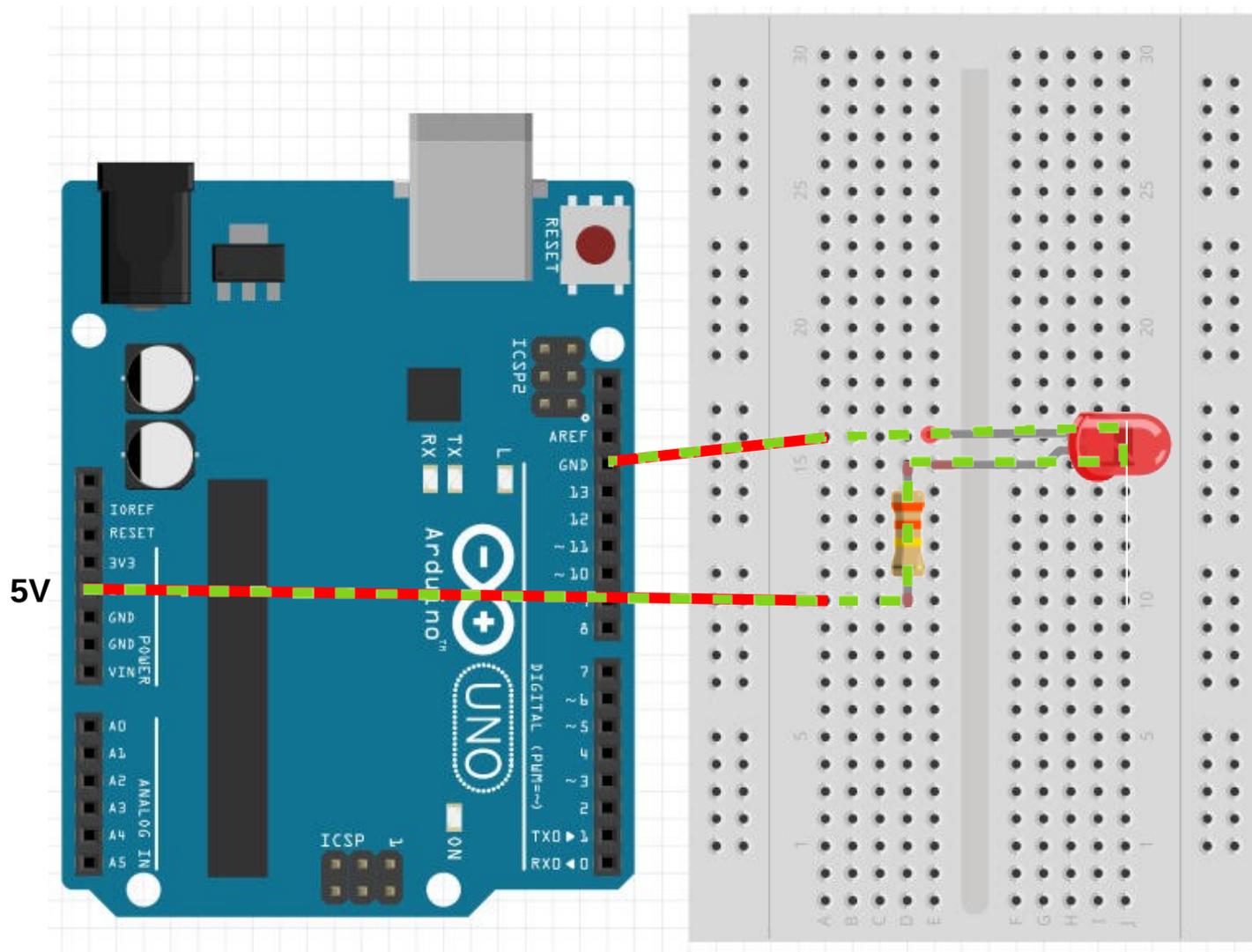


This is how the electricity is flowing

From...

- 5V to...
- Resistor to...
- LED to...
- GND

Connecting an LED

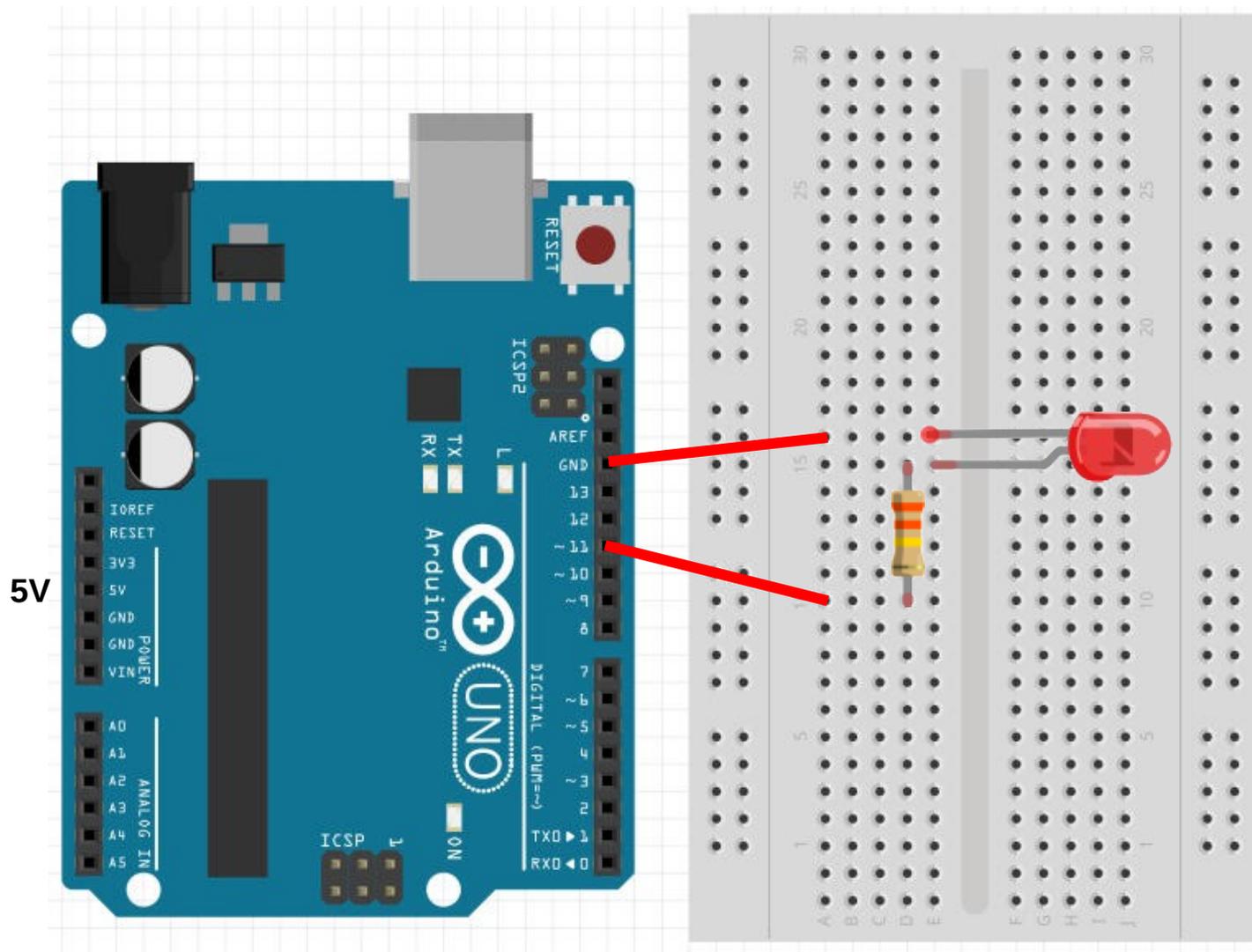

Controlling the LED

To control the LED, we need to connect it to an output pin instead of 5V.

- Disconnect it from 5V.
- Connect it to Pin 11.

Why the resistor?

- Arduino pins provide **5V**
- Different color LEDs require different voltages
 - Red, Yellow, Infra-red: **1.8V**
 - Blue, White, UV: **3.3V**
 - Green: Depends. Try **1.8V** first.
- **Resistor helps to reduce the voltage**
- What happens when you connect 5V to a Red LED without a resistor?

Challenges


- 1) Program the connected LED blink continuously
- 2) Program the connected LED to blink at a varying rate (slow-fast-slow)

Exercise 1b


External Inputs

A POSTERIORI
Play · Experience · Learn

Push Button Switch

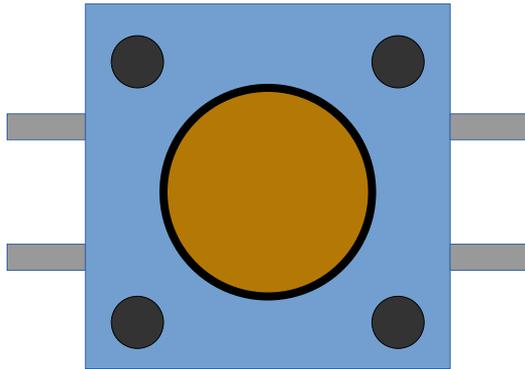


External View

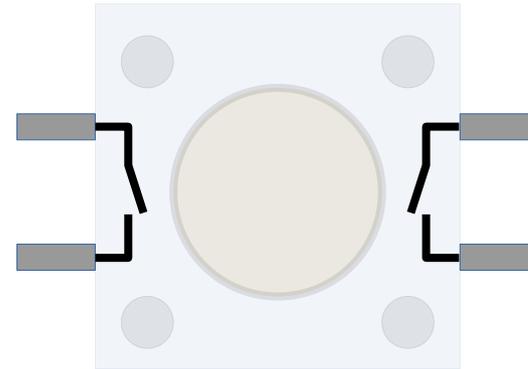


Internal View

Connecting a Switch

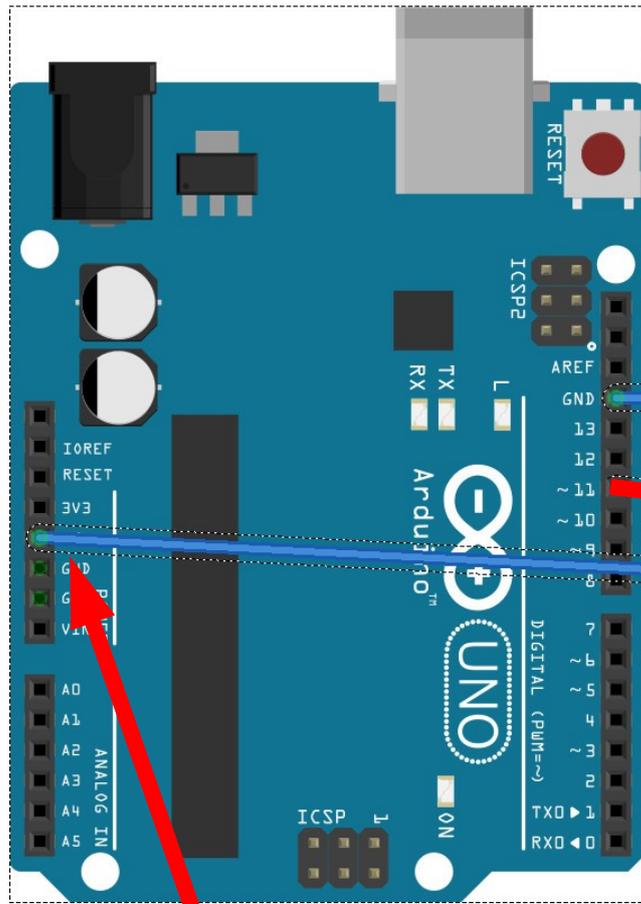

Connected to 5V

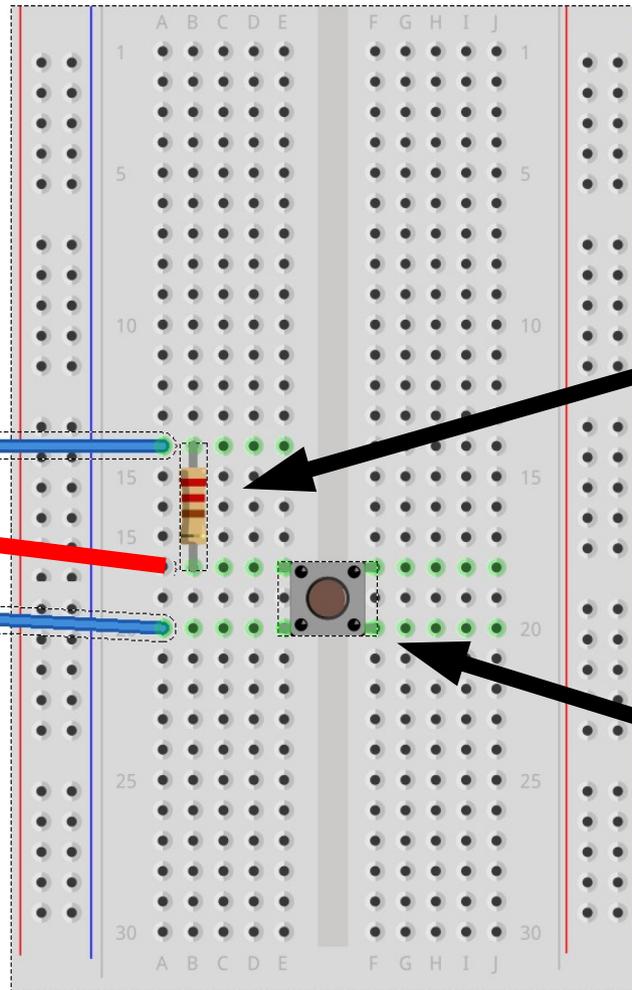

Make these connections

Resistor

Value isn't as important as before. Recommend to pick 1000 ohm, but most other values will do as well.


Push button switch

Connects the adjacent pins. Only need to use one side...

Connecting a Switch

- When switch is open...
- Pin 11 is connected to 0V via the resistor
- Pin 11 not connected to 5V


Voltage of pin 11
= 0 V
= False
= Low

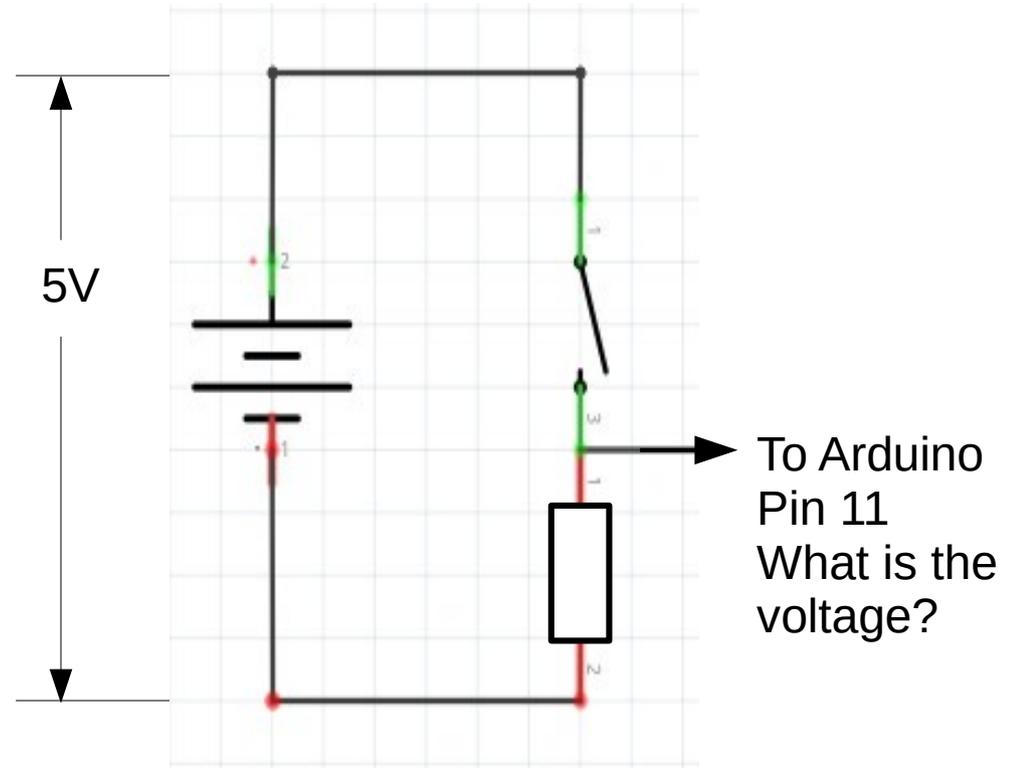

Connecting a Switch

- When switch is closed...
- Pin 11 is connected to 0V via the resistor
- Pin 11 is connected to 5V directly

Voltage of pin 11
= 5 V
= True
= High

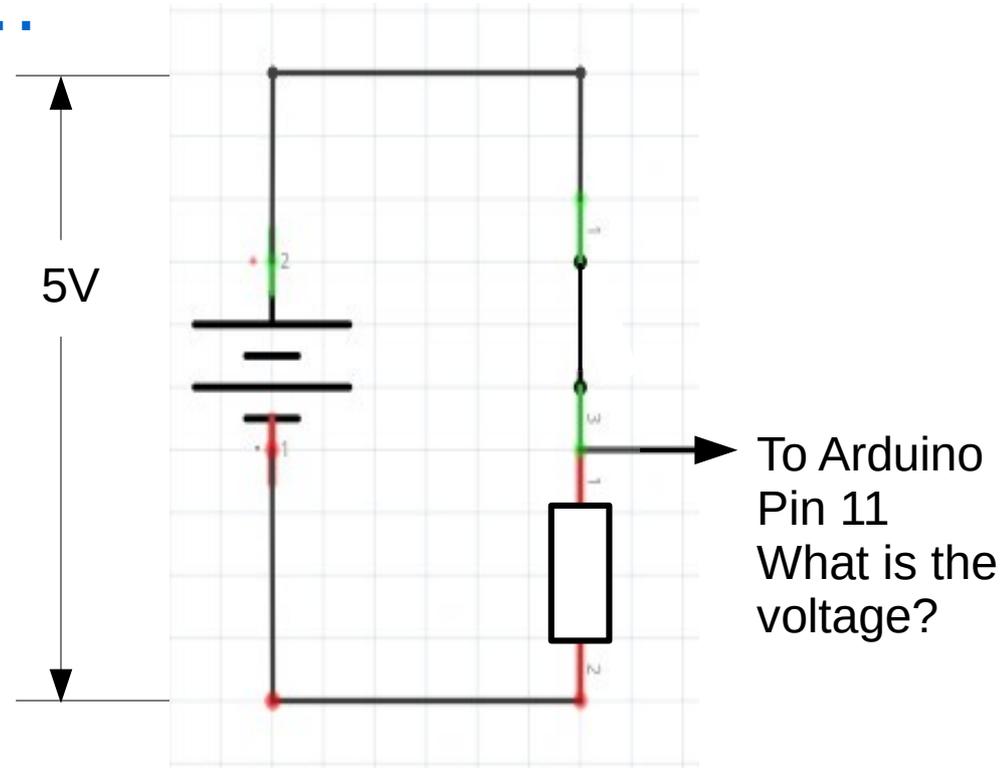


Connecting a Switch

- This resistor is call a **pull-down resistor**, because it pulls the voltage down to 0V when the switch is open
- We can also connect the resistor to 5V and the switch to Gnd. This is call a **pull-up resistor**.

Connecting a Switch

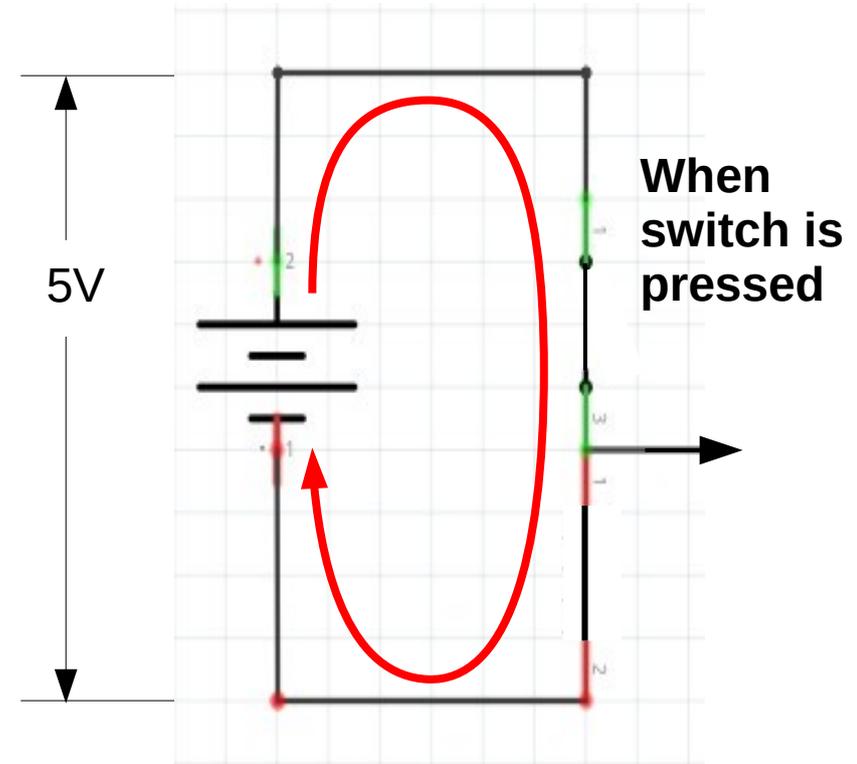- Can we connect the switch to Gnd without a resistor?
 - NO! Without the resistor, we will have a short circuit when the switch is pressed



Positive connected directly to negative.
Short circuit!

Challenges

- 1) Make an LED blink rapidly for 2 seconds when the button is pressed
- 2) Make an LED toggle between on and off when the button is pressed

Copyright

- Created by A Posteriori LLP
- Visit <http://aposteriori.com.sg/> for more tips and tutorials
- This work is licensed under a Creative Commons Attribution-ShareAlike 4.0 International License.

