

Next few sessions

- 11 Nov
 - H-bridge
 - Soldering
- 18 Nov ???
 - Gyro
 - Construction
- Date ???
 - PID (Proportional)
 - Wireless
- Date ???
 - Pressure sensor
 - PID (Proportional + Derivative)

Plan for today

- Watch and discuss video
- Form teams
- 2-Wheel robot
 - H-Bridge driver
 - Soldering
- Discuss underwater robot design

Videos


Radio Transmitter and Receiver



Radio Transmitter and Receiver



Radio Transmitter and Receiver

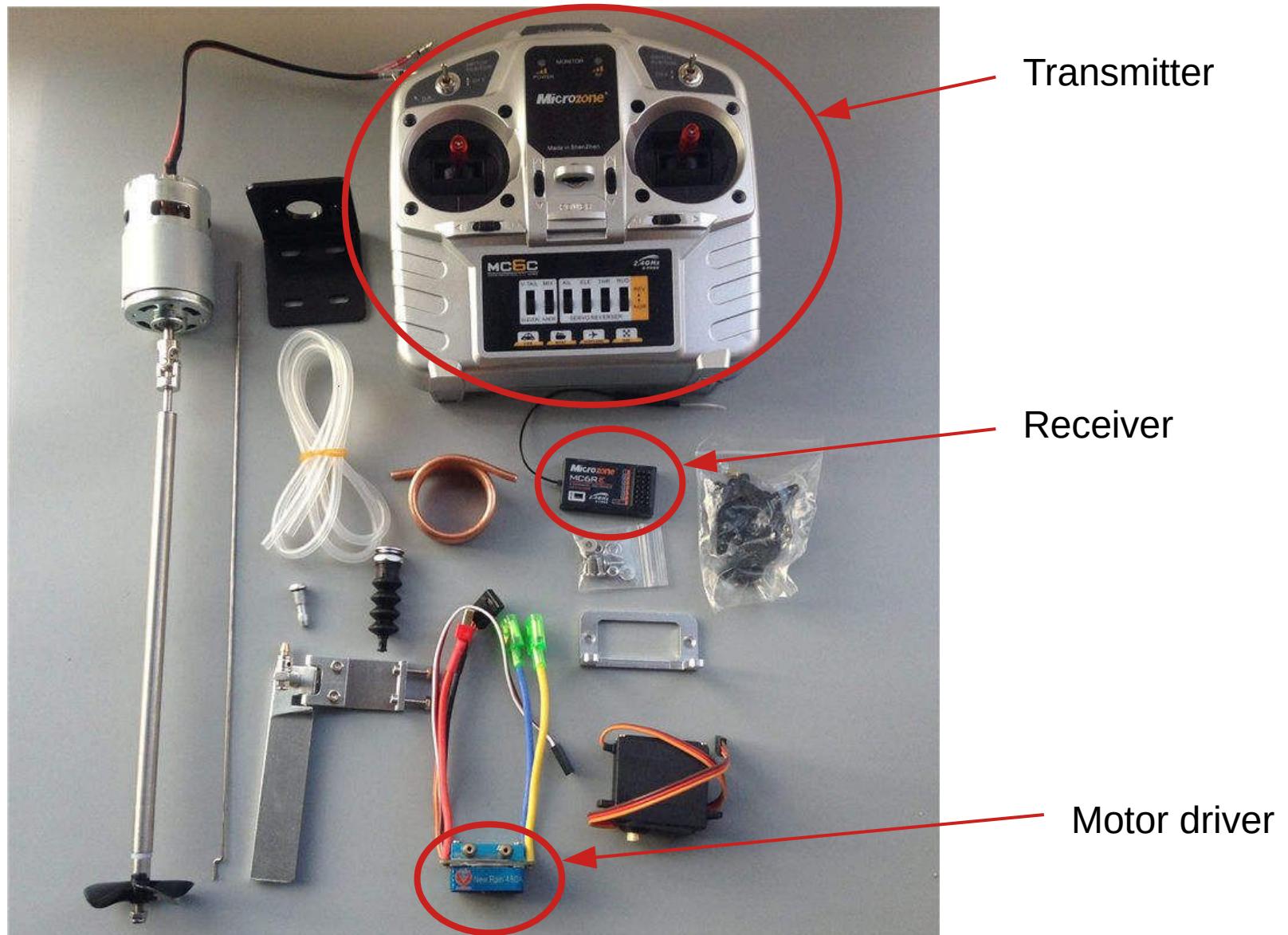


Form Teams

- Not more than 4 in a team and at least 2
- Decide by end of the session
- Can discuss later during soldering...


H-Bridge

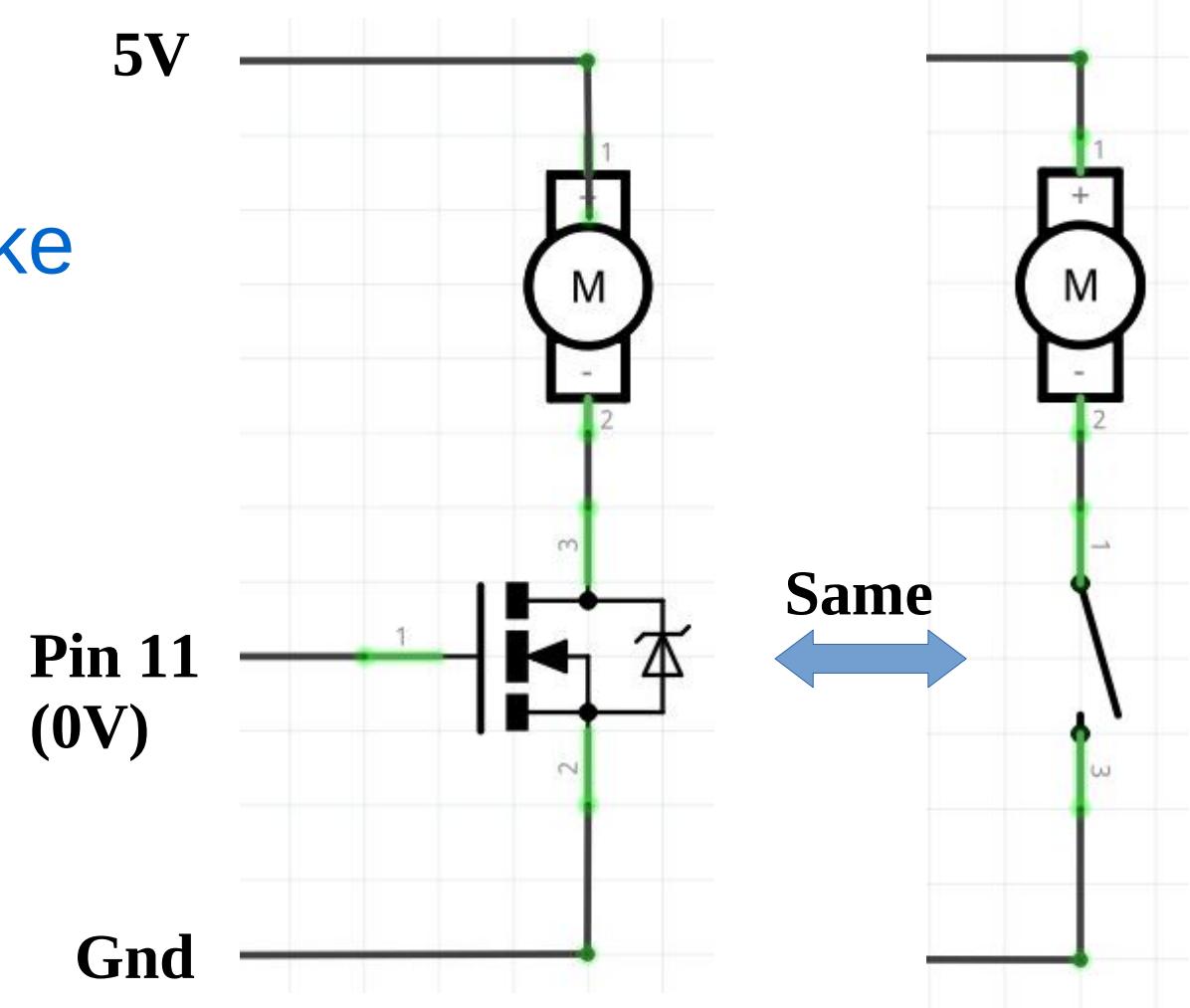- Refresher...
- Transistors acts like a switch
- Can turn motor on and off
- How to reverse?




H-Bridge

- Use a H-Bridge...

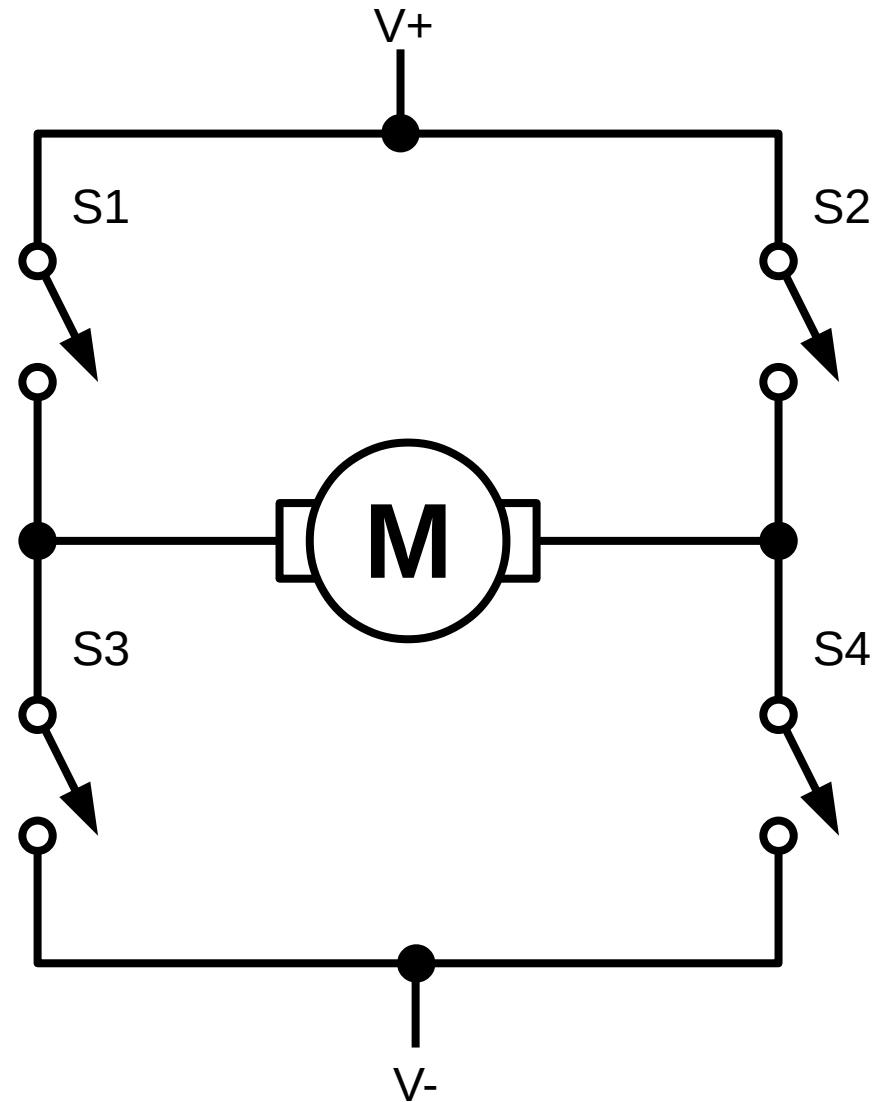


H-Bridge

- ...which looks kind of like a “H”

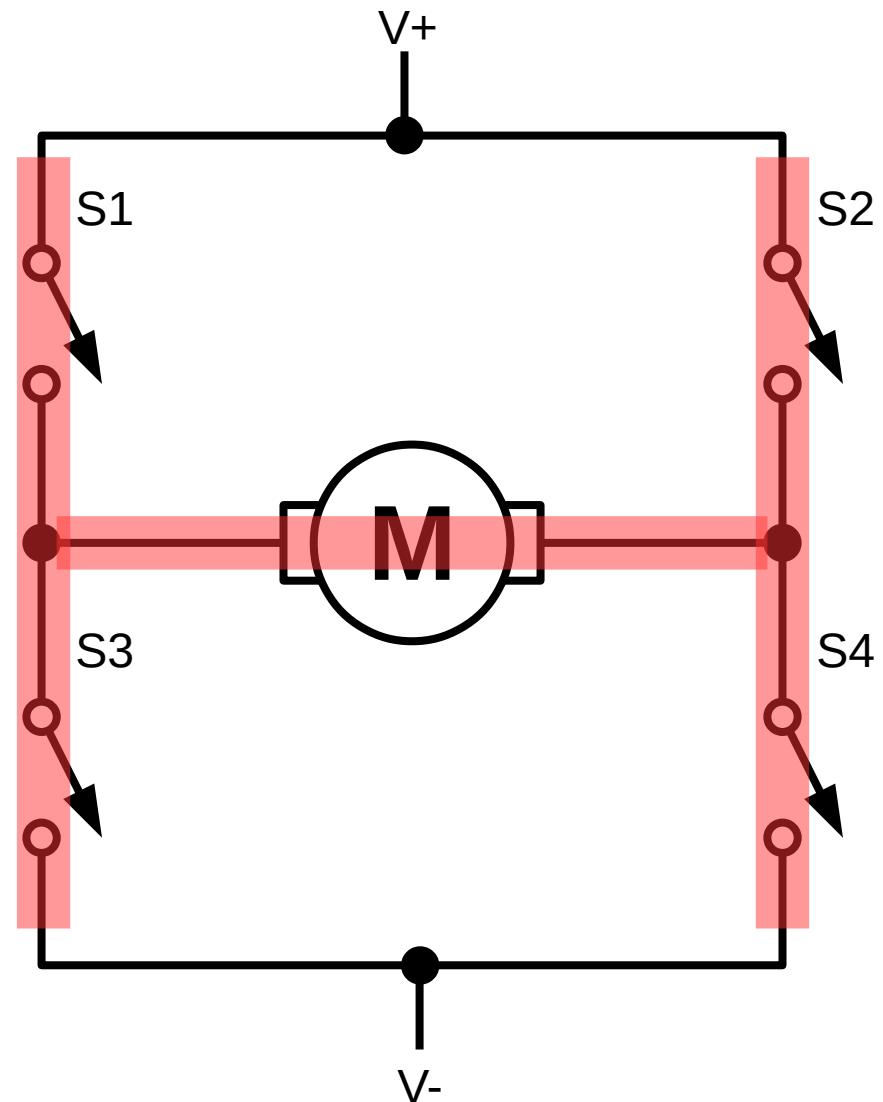


H-Bridge

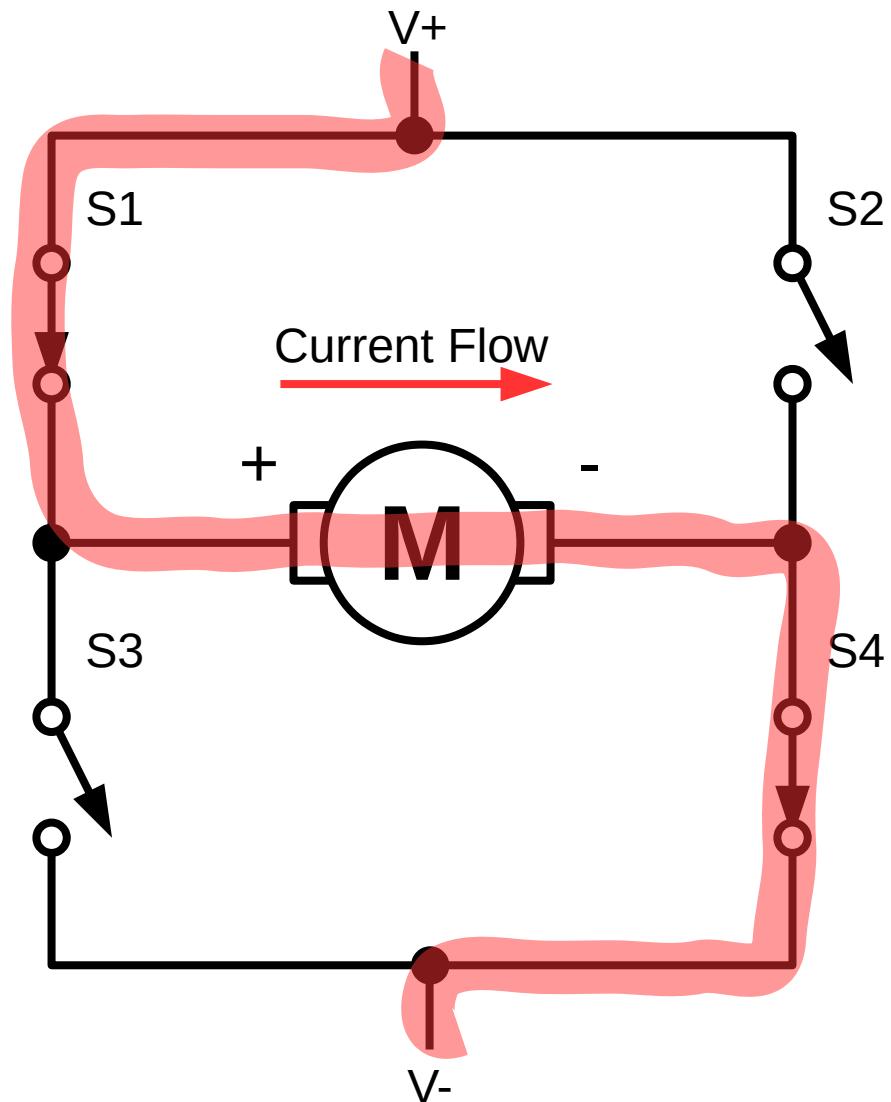- **Direction 1**
 - On: S1 & S4
 - Off: S2 & S3




H-Bridge

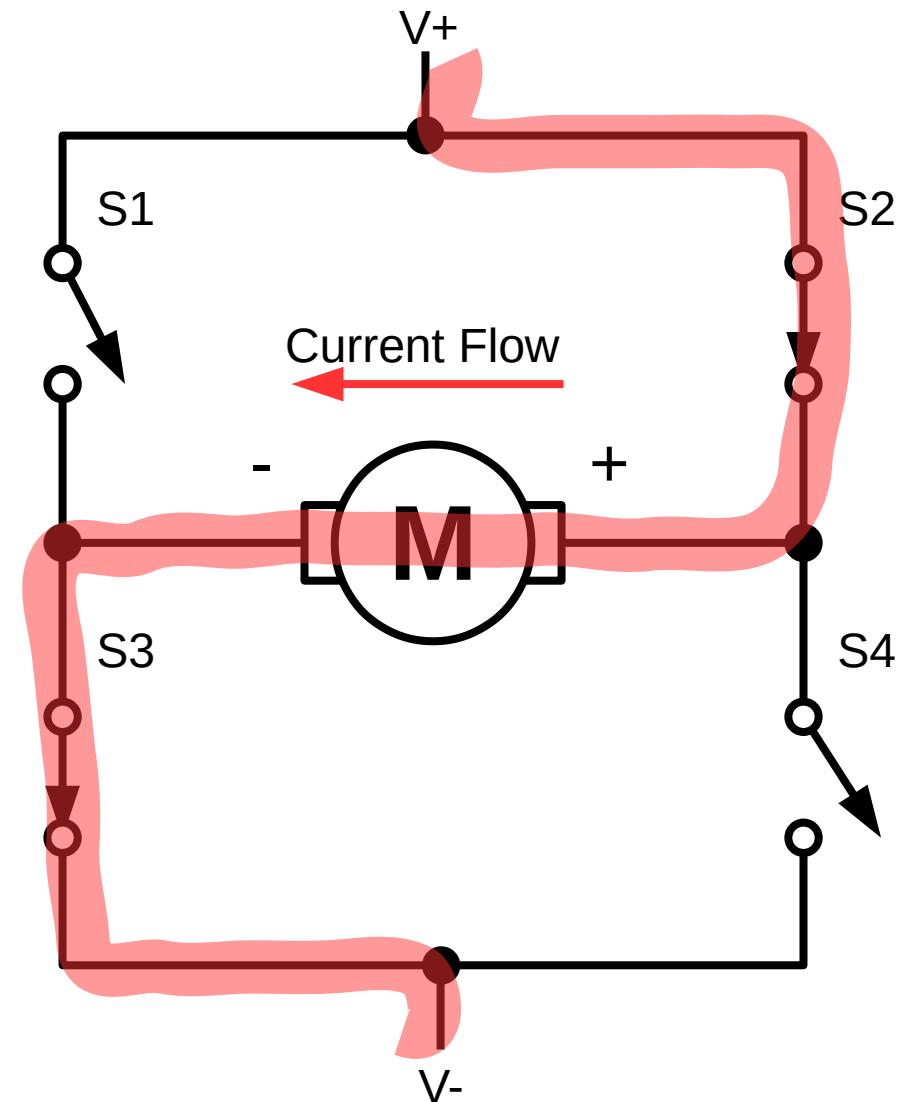- **Direction 2**
 - On: S2 & S3
 - Off: S1 & S4




H-Bridge

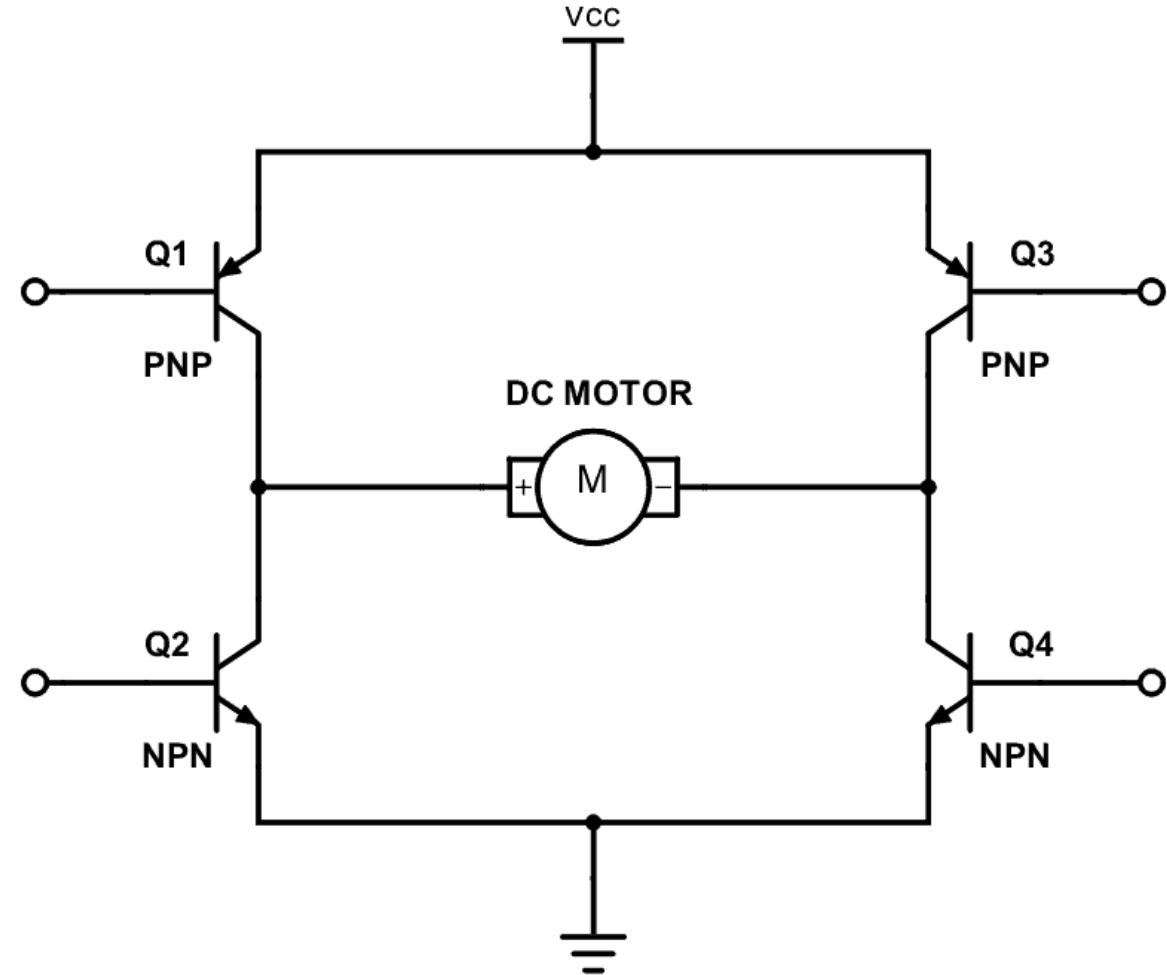- Replace switches with transistors...
- Combine some of the controls...
 - eg. Q1 & Q4 can be merged into one





H-Bridge

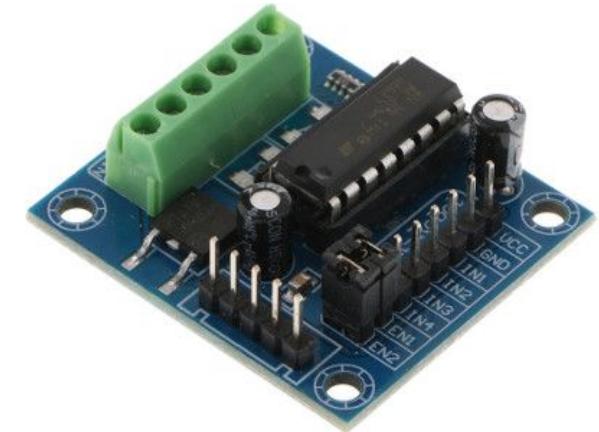- H-Bridge drivers contains...
 - H-Bridge circuit
 - Combines some controls
 - A few extras (varies)




This is the one
we'll be using

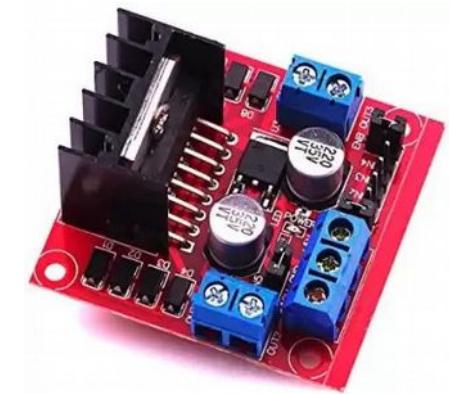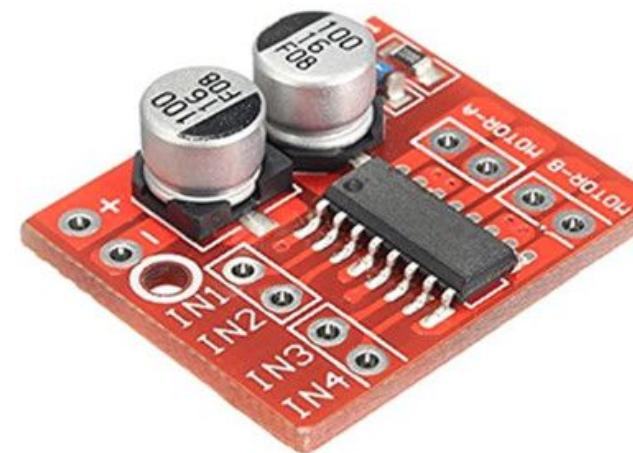

H-Bridge

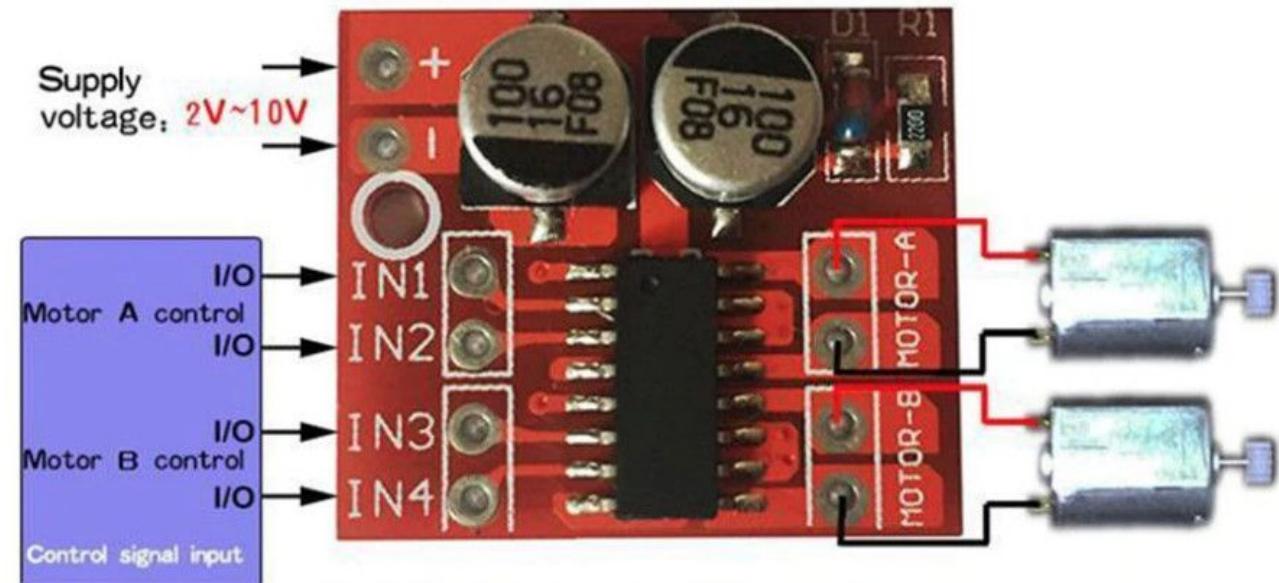- Contains 2 H-bridges
 - Can control 2 motors
- Max:
 - 1.5A
 - 10V
- Needs soldering




Two independent drive DC motor;

INx control signal input, signal voltage range 1.8–7V;

IN1, IN2 control the motor A; IN2, IN3 control motor B;

H-Bridge

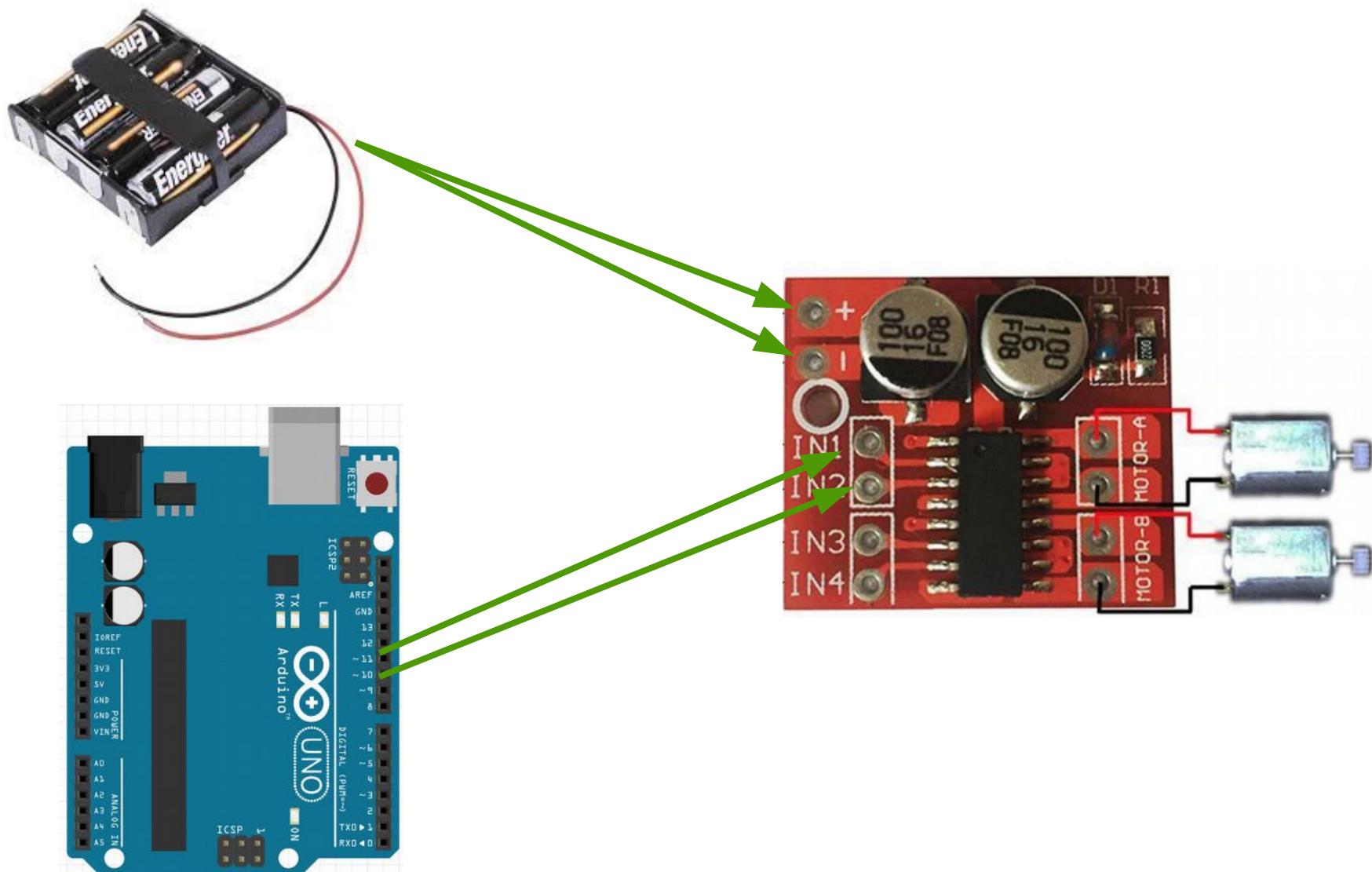


H-Bridge

IN1 : HIGH



IN2 : LOW

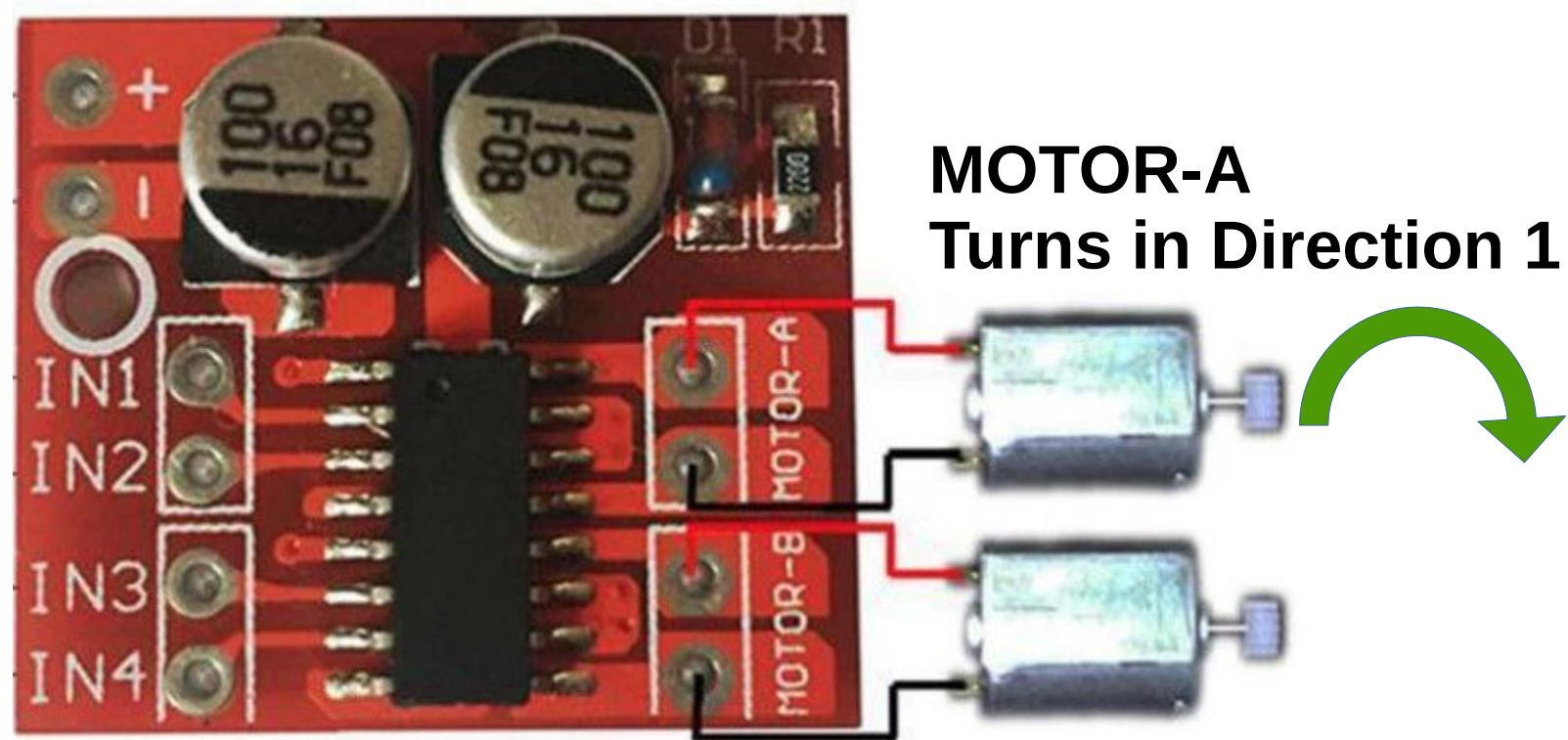


H-Bridge

IN1 : LOW



IN2 : HIGH

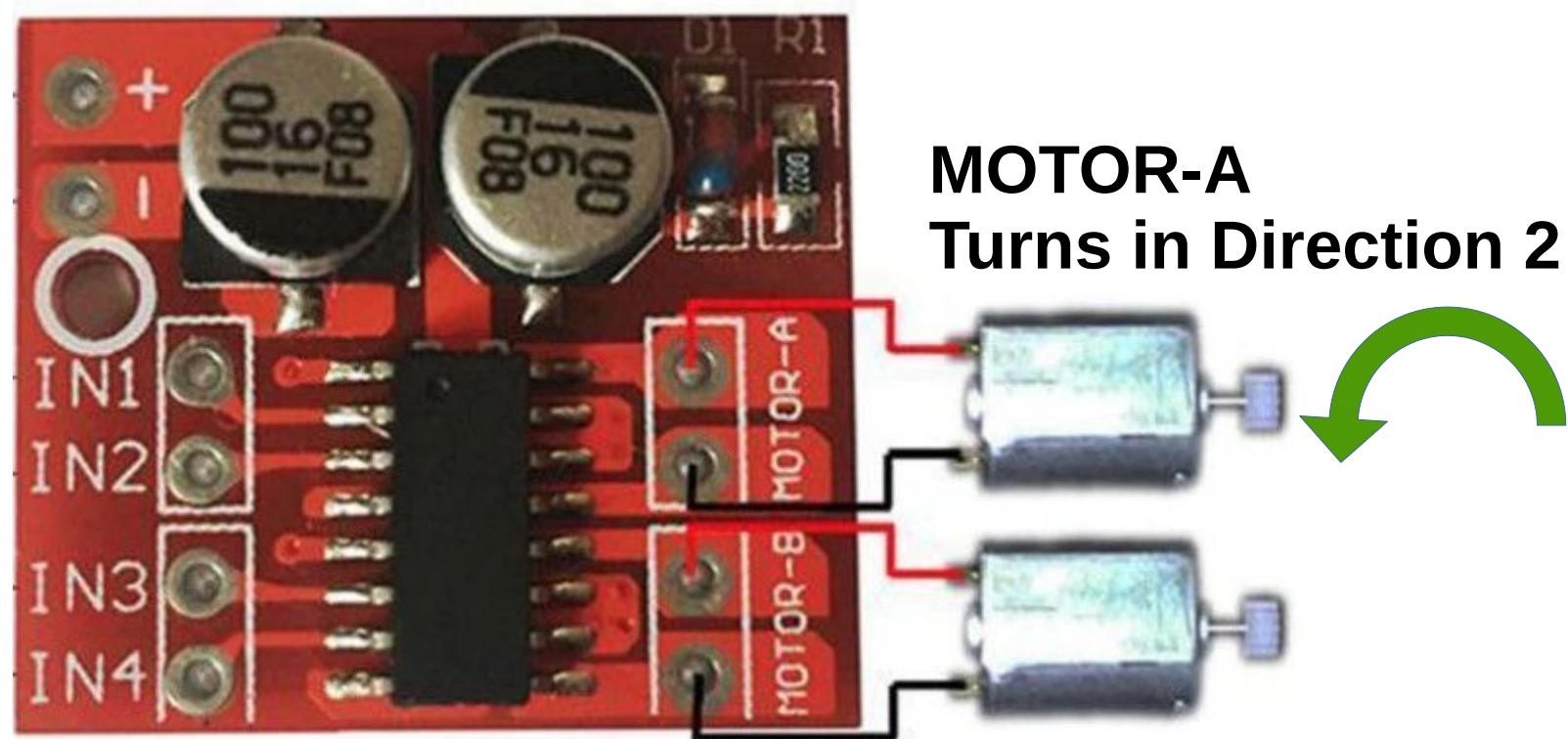


H-Bridge

IN1 : LOW



IN2 : LOW

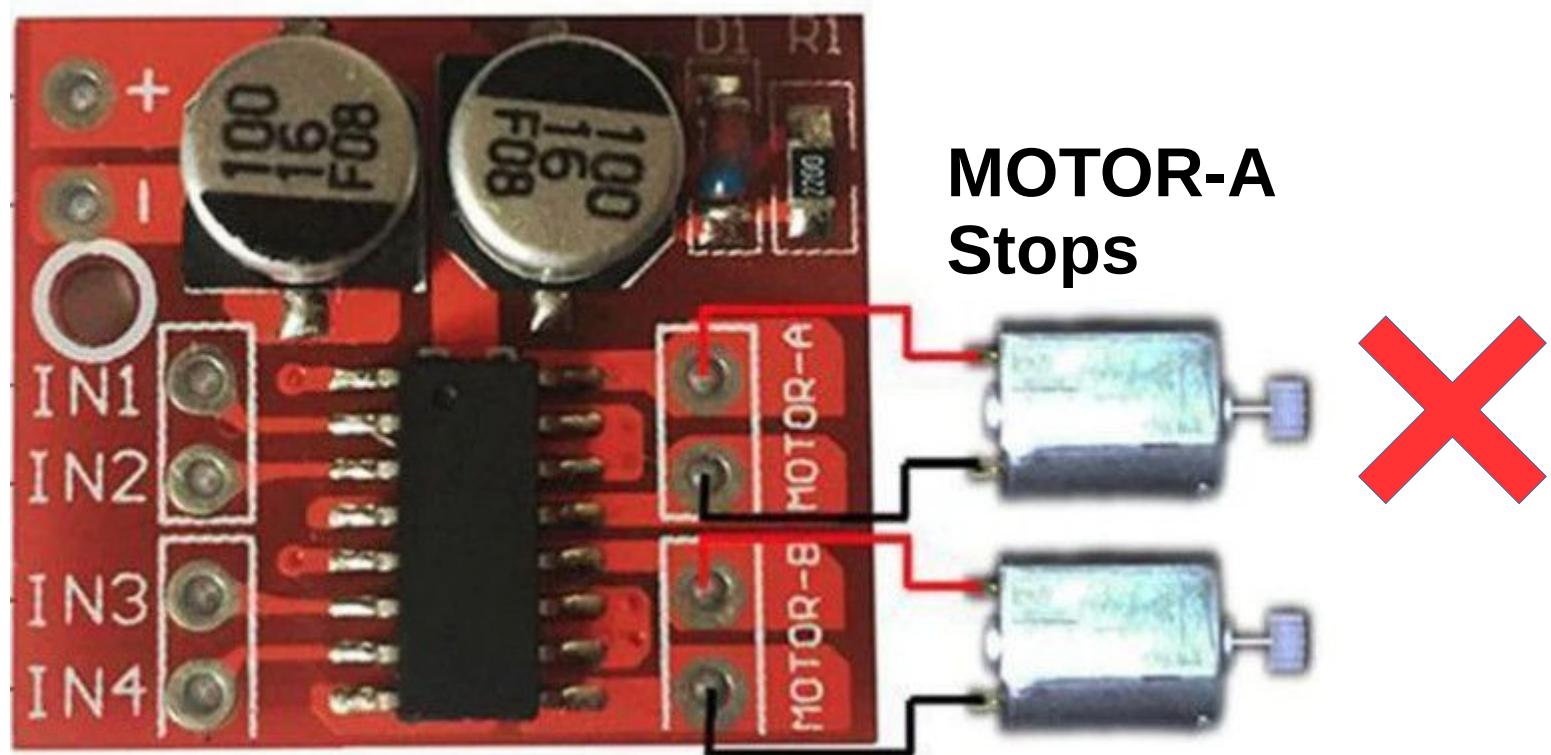


H-Bridge

IN1 : HIGH



IN2 : HIGH

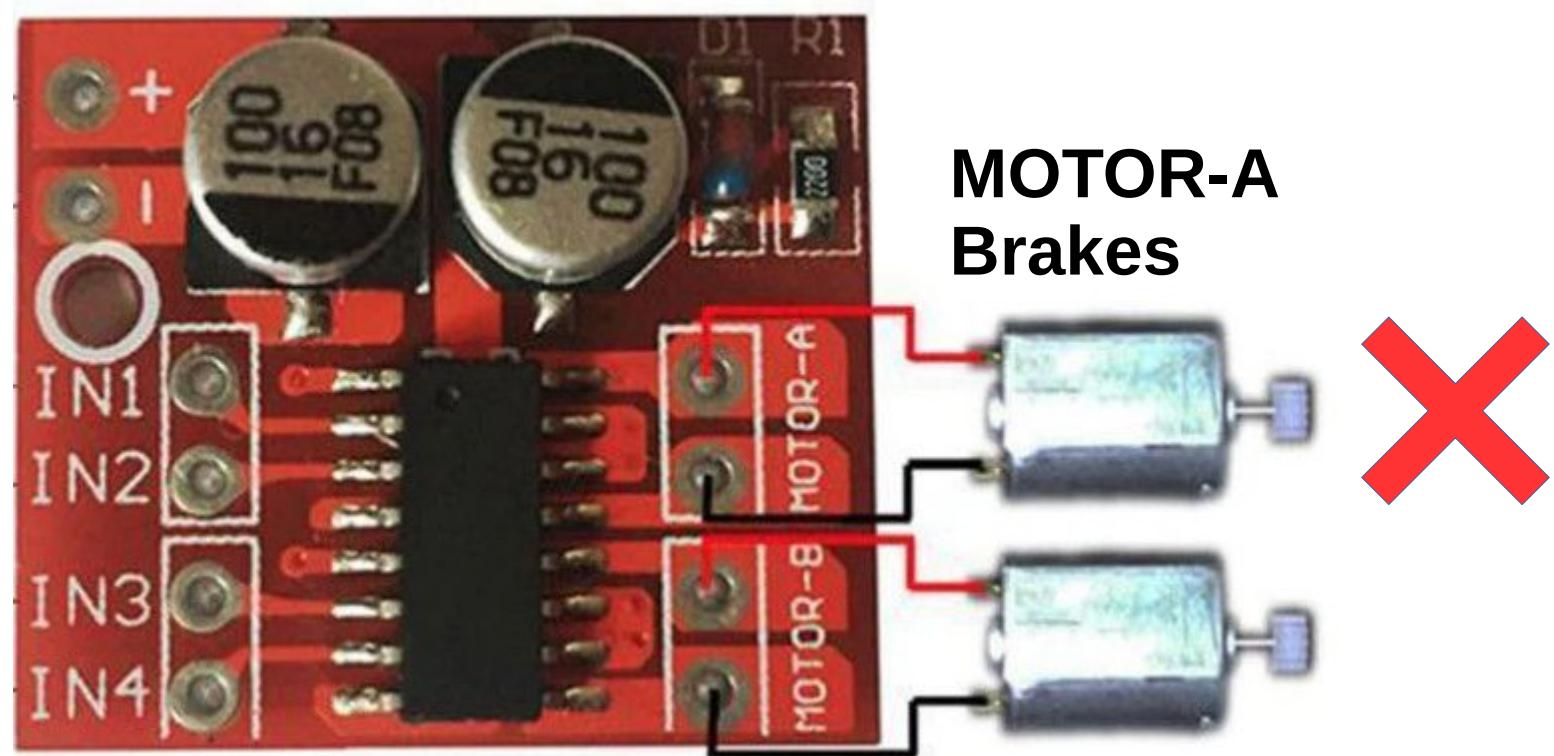

H-Bridge

- Can control direction by choosing which pin to turn on
- Can control speed using PWM (...just like what we did before using the transistor)

Forward at full power*

```
analogWrite(11, 255);  
analogWrite(10, 0);
```

Reverse at half power*


```
analogWrite(11, 0);  
analogWrite(10, 127);
```

* Assumes pin 10 & 11 are connected to H-bridge driver. Direction depends on wiring.

Soldering

- Limited number of soldering irons
- While waiting...
 - Plan your teams
 - Discuss your underwater robot design

Underwater Robot Design

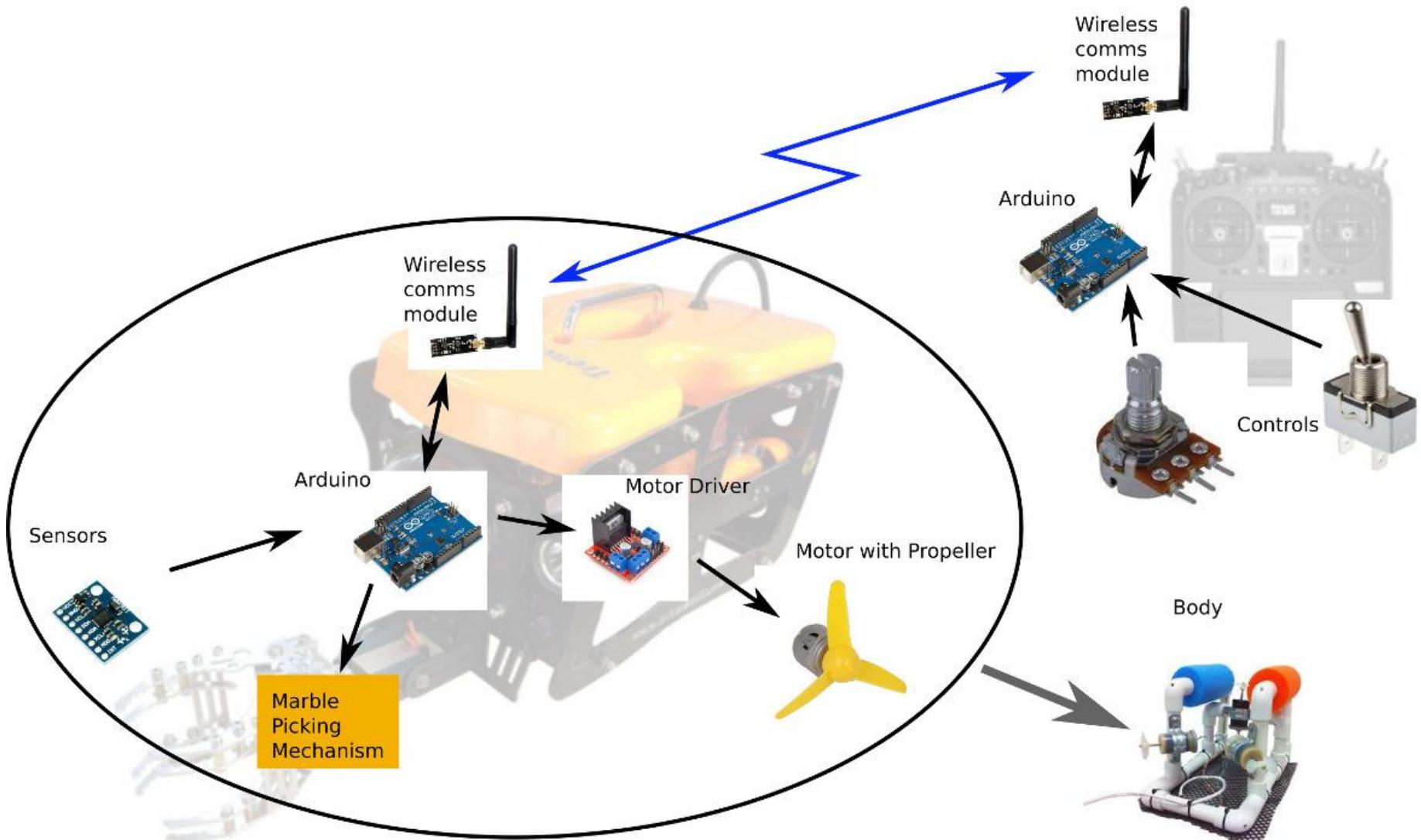

Contact

- Email me at any time if you need advice:
- cort@aposteriori.com.sg

Copyright

- Created by A Posteriori LLP
- Visit <http://aposteriori.com.sg/> for more tips and tutorials
- This work is licensed under a Creative Commons Attribution-ShareAlike 4.0 International License.

